



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 30: MODELING MEMORY

PROF. INDRANIL SENGUPTA

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

How to Model Memory?

- Memory is typically included by instantiating a pre-designed module from a design library.
- Alternatively, we can model memories using two-dimensional arrays.
 - Array of register variables (behavioral model).
 - Mainly used for simulation purposes.
 - Even used for the synthesis of small-size memories.



Typical Example

```
module memory_model ( ..... )  
    ...  
    reg [7:0] mem [0:1023];  
    ...  
endmodule
```

```
module memory_model ( ..... )  
    reg [7:0] mem [0:1023];  
    initial begin  
        mem[0] = 8'b01001101;  
        mem[4] = 8'b00000000;  
    end  
endmodule
```

- Each memory word is of type [7:0], i.e. 8 bits.
- The memory words can be accessed as `mem[0]`, `mem[1]`, ..., `mem[1023]`.



How to Initialize Memory?

- By reading memory data patterns from a specified disk file.
 - Used for simulation.
 - Used in test benches.

- Two Verilog functions can be used:

`$readmemb (filename, memname, startaddr, stopaddr)`

(Data is read in binary format)

`$readmemh (filename, memname, startaddr, stopaddr)`

(Data is read in hexadecimal format)

- If “*startaddr*” and “*stopaddr*” are omitted, the entire memory is read.



Example 1: Initializing a memory from file

```
module memory_model ( ..... );  
    reg [7:0] mem[0:1023];  
    initial  
        begin  
            $readmemh ("mem.dat", mem);  
        end  
endmodule
```

```
module memory_model ( ..... );  
    reg [7:0] mem[0:1023];  
    initial  
        begin  
            $readmemb ("mem.dat", mem,  
                        200, 50);  
        end  
endmodule
```



Example 2: Single-port RAM with synchronous read/write

```
module ram_1 (addr, data, clk, rd, wr, cs);
  input  [9:0] addr;    input  clk, rd, wr, cs;
  inout  [7:0] data;
  reg [7:0] mem [1023:0]; reg [7:0] d_out;

  assign data = (cs && rd) ? d_out : 8'bz;
  always @(posedge clk)
    if (cs && wr && !rd) mem[addr] = data;
  always @(posedge clk)
    if (cs && rd && !wr) d_out = mem[addr];
endmodule
```



Example 3: Single-port RAM with asynchronous read/write

```
module ram_2 (addr, data, rd, wr, cs);
    input  [9:0] addr;    input  rd, wr, cs;
    inout  [7:0] data;
    reg [7:0] mem[1023:0];    reg [7:0] d_out;

    assign data = (cs && rd) ? d_out : 8'bz;
    always @(addr or data or rd or wr or cs)
        if (cs && wr && !rd) mem[addr] = data;
    always @(addr or rd or wr or cs)
        if (cs && rd && !wr) d_out = mem[addr];
endmodule
```



Example 4: A ROM / EPROM

```
module rom (addr, data, rd_en, cs);  
    input  [2:0] addr;    input  rd_en, cs;  
    output reg [7:0] data;  
    always @(addr or rd_en or cs)  
        case (addr)  
            0:    data = 22;  
            1:    data = 45;  
            .....  
            7:    data = 12;  
        endcase  
endmodule
```




An Important Point to Note

- Some simulation or synthesis tools give inconsistent behavior when using the “*inout*” data type.
 - Such “*inout*” bidirectional data should be avoided.
- A better way to design a memory unit is to keep the data input and data output bus signal lines separate.
 - An example memory description with separate data buses is shown on the next slide.



Example 4

 


```
module ram_3 (data_out, data_in, addr, wr, cs);  
    parameter addr_size = 10, word_size = 8,  
              memory_size = 1024;  
    input [addr_size-1:0] addr;  
    input [word_size-1:0] data_in;  
    input wr, cs;  
    output [word_size-1:0] data_out;  
    reg [word_size-1:0] mem [memory_size-1:0];  
  
    assign data_out = mem[addr];  
    always @(wr or cs)  
        if (wr) mem[addr] = data_in;  
endmodule
```



- For bidirectional data bus, tristate buffers can be included explicitly.
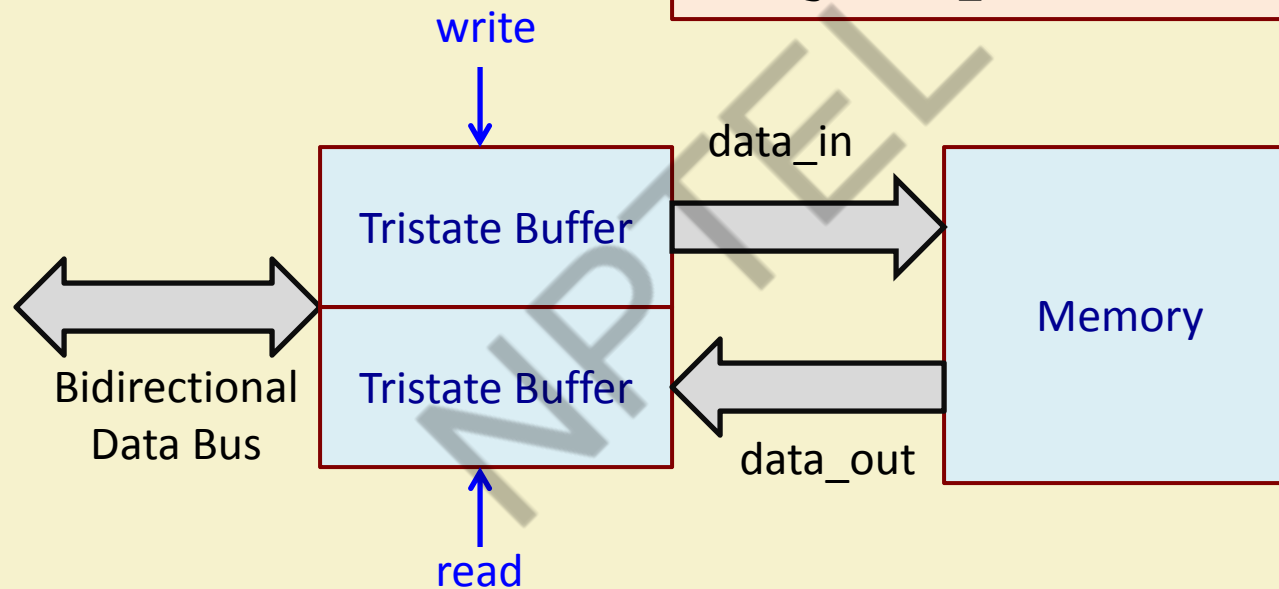
```
tri [7:0] Bus;  
wire [7:0] data_out, data_in;  
assign Bus = read ? data_out : 8'hzz;  
assign data_in = write ? Bus : 8'hzz;
```



Simple Test Bench using ram_3

```
module RAM_test;
  reg [9:0] address;
  wire [7:0] data_out;
  reg [7:0] data_in;
  reg write, select;
  integer k, myseed;

  ram_3 RAM (data_out, data_in, address, write, select);

  initial
    begin
      for (k=0; k<=1023; k=k+1)
        begin
          address = k;
          data = (k + k) % 256; read = 0; write = 1; select = 1;
          #2 write = 0; select = 0;
        end
    end
end
```



```

repeat (20)
  begin
    #2 address = $random(myseed) % 1024;
    write = 0; select = 1;
    $display ("Address: %5d, Data: %4d", address,
              data);
    #2 select = 0;
  end
end

initial myseed = 35;
endmodule

```

```

Address:    0, Data:    0
Address:  960, Data:  128
Address:  482, Data:  196
Address:  693, Data:  106
Address:  246, Data:  236
Address:  228, Data:  200
Address:  148, Data:   40
Address:  767, Data:  254
Address:  355, Data:  198
Address:  259, Data:    6
Address:   21, Data:   42
Address:  872, Data:  208
Address:  758, Data:  236
Address:  193, Data:  130
Address:  909, Data:   26
Address:  632, Data:  240
Address:  719, Data:  158
Address:  214, Data:  172
Address:   67, Data:  134
Address:  908, Data:   24

```



END OF LECTURE 30



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

14



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 31: MODELING REGISTER BANKS

PROF. INDRANIL SENGUPTA

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING


Introduction

- A register bank or register file is a group of registers, any of which can be randomly accessed.
 - Commonly used in computers to store the user-accessible registers.
 - For example, in the MIPS32 processor, there are 32 32-bit registers, referred to as *R0, R1, ..., R31*.
- Can be implemented in Verilog as independent registers, or as an array of registers similar to a memory.
- Registers banks often allow concurrent accesses.
 - MIPS32 allows *2 register reads and 1 register write every clock cycle*.



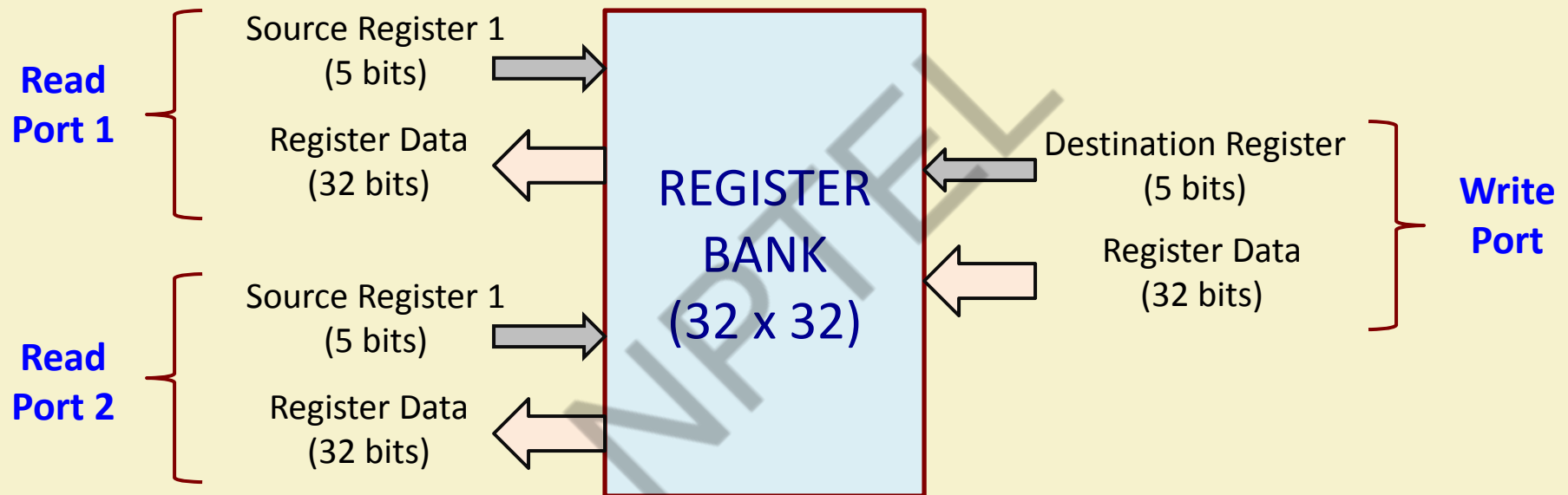- We show various ways of designing a register bank that supports two reads and one write simultaneously.
 - It is assumed that the same register is not read and written simultaneously.





```
// 4 x 32 register file
```

```
module regbank_v1 (rdData1, rdData2, wrData, sr1, sr2, dr, write, clk);  
    input clk, write;  
    input [1:0] sr1, sr2, dr; // Source and destination registers  
    input [31:0] wrData;  
    output reg [31:0] rdData1, rdData2;  
    reg [31:0] R0, R1, R2, R3;  
  
    always @(*)  
        begin  
            case (sr1)  
                0: rdData1 = R0;  
                1: rdData1 = R1;  
                2: rdData1 = R2;  
                3: rdData1 = R3;  
                default: rdData1 = 32'hxxxxxxxx;  
            endcase  
        end  
end
```



```

always @(*)
begin
    case (sr2)
        0: rdData2 = R0;
        1: rdData2 = R1;
        2: rdData2 = R2;
        3: rdData2 = R3;
        default: rdData2 = 32'hxxxxxxxx;
    endcase
end
always @(posedge clk)
begin
    if (write)
        case (dr)
            0: R0 <= wrData;
            1: R1 <= wrData;
            2: R2 <= wrData;
            3: R3 <= wrData;
        endcase
    end
endmodule

```

This way of modeling is feasible if the number of registers is small.



```
// 4 x 32 register file
```

```
module regbank_v2 (rdData1, rdData2, wrData, sr1, sr2, dr, write, clk);  
    input clk, write;  
    input [1:0] sr1, sr2, dr; // Source and destination registers  
    input [31:0] wrData;  
    output [31:0] rdData1, rdData2;  
    reg [31:0] R0, R1, R2, R3;  
  
    assign rdData1 = (sr1 == 0) ? R0 :  
                     (sr1 == 1) ? R1 :  
                     (sr1 == 2) ? R2 :  
                     (sr1 == 3) ? R3 : 0;  
    assign rdData2 = (sr2 == 0) ? R0 :  
                     (sr2 == 1) ? R1 :  
                     (sr2 == 2) ? R2 :  
                     (sr2 == 3) ? R3 : 0;  
  
    always @(posedge clk)  
        begin  
            if (write)  
                case (dr)  
                    0: R0 <= wrData;  
                    1: R1 <= wrData;  
                    2: R2 <= wrData;  
                    3: R3 <= wrData;  
                endcase  
        end  
endmodule
```



```
// 32 x 32 register file
module regbank_v3 (rdData1, rdData2, wrData, sr1, sr2, dr, write, clk);
    input clk, write;
    input [4:0] sr1, sr2, dr; // Source and destination registers
    input [31:0] wrData;
    output [31:0] rdData1, rdData2;

    reg [31:0] regfile[0:31];

    assign rdData1 = regfile[sr1];
    assign rdData2 = regfile[sr2];

    always @(posedge clk)
        if (write) regfile[dr] <= wrData;
endmodule
```



```
// 32 x 32 register file with reset facility
```

```
module regbank_v4 (rdData1, rdData2, wrData, sr1, sr2, dr, write, reset, clk);  
    input clk, write, reset;  
    input [4:0] sr1, sr2, dr;    // Source and destination registers  
    input [31:0] wrData;  
    output [31:0] rdData1, rdData2;  
    integer k;  
  
    reg [31:0] regfile[0:31];  
  
    assign rdData1 = regfile [sr1];  
    assign rdData2 = regfile [sr2];  
  
    always @(posedge clk)  
        begin  
            if (reset) begin  
                for (k=0; k<32; k=k+1) begin  
                    regfile[k] <= 0;  
                end  
            end  
            else begin  
                if (write)  
                    regfile[dr] <= wrData;  
            end  
        end  
endmodule
```



A test bench to verify operation of the register file

```
module regfile_test;

reg [4:0] sr1, sr2, dr;
reg[31:0] wrData;
reg write, reset, clk;
wire [31:0] rdData1, rdData2;
integer k;

regbank_v4 REG (rdData1, rdData2, wrData, sr1, sr2, dr, write, reset, clk);

initial clk = 0;

always #5 clk = !clk;

initial
begin
    $dumpfile ("regfile.vcd"); $dumpvars (0, regfile_test);
    #1 reset = 1; write = 0;
    #5 reset = 0;
end
```




```

initial
begin
  #7
  for (k=0; k<32; k=k+1)
    begin
      dr = k; wrData = 10* k; write = 1;
      #10 write = 0;
    end

  #20
  for (k=0; k<32; k=k+2)
    begin
      sr1 = k; sr2 = k+1;
      #5;
      $display ("reg[%2d] = %d, reg[%2d] = %d", sr1, rdData1, sr2, rdData2);
    end

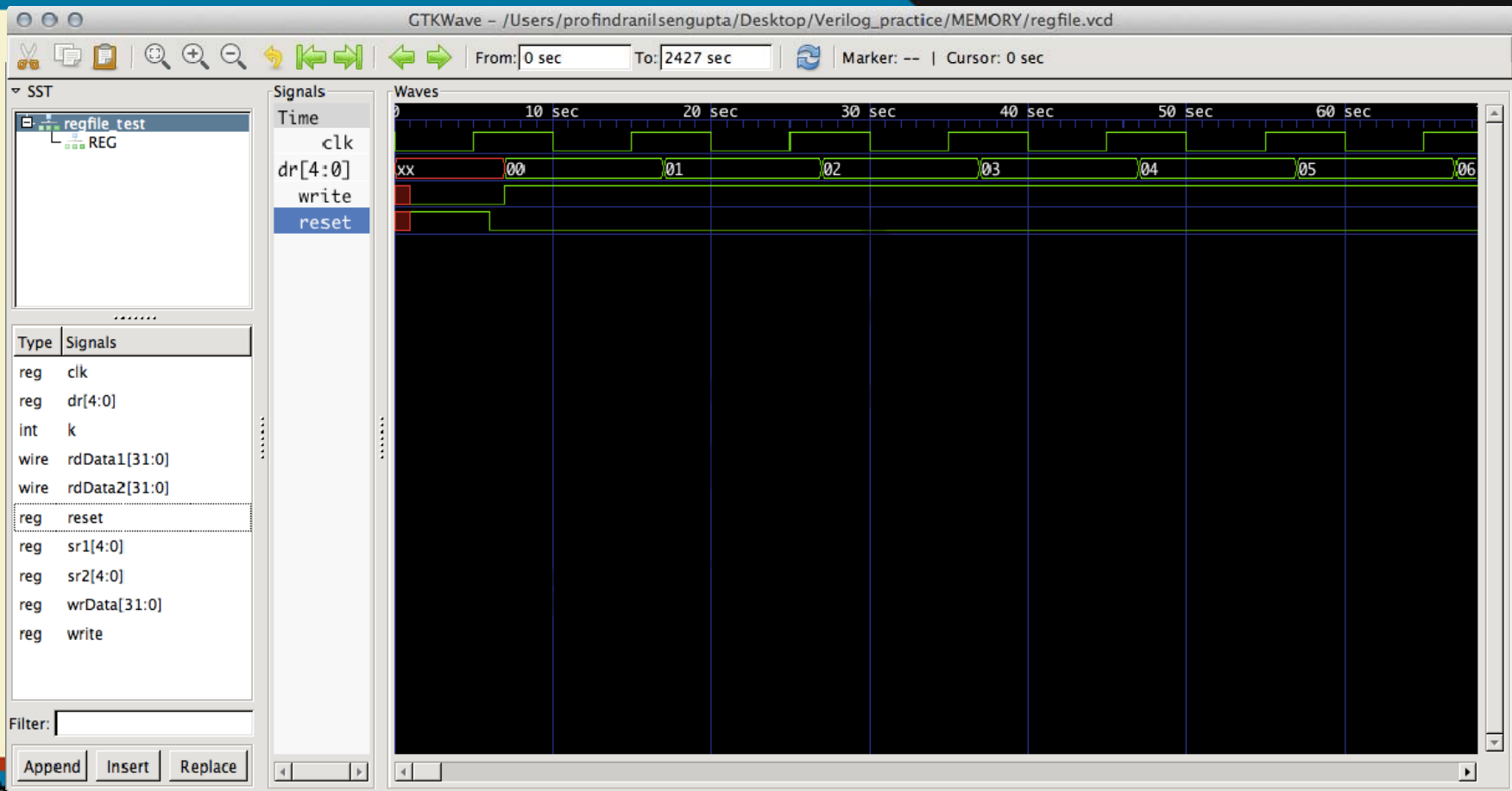
  #2000 $finish;
end
endmodule


```



```
reg[ 0] =          0, reg[ 1] =          10
reg[ 2] =         20, reg[ 3] =          30
reg[ 4] =         40, reg[ 5] =          50
reg[ 6] =         60, reg[ 7] =          70
reg[ 8] =         80, reg[ 9] =          90
reg[10] =        100, reg[11] =         110
reg[12] =        120, reg[13] =         130
reg[14] =        140, reg[15] =         150
reg[16] =        160, reg[17] =         170
reg[18] =        180, reg[19] =         190
reg[20] =        200, reg[21] =         210
reg[22] =        220, reg[23] =         230
reg[24] =        240, reg[25] =         250
reg[26] =        260, reg[27] =         270
reg[28] =        280, reg[29] =         290
reg[30] =        300, reg[31] =         310
```





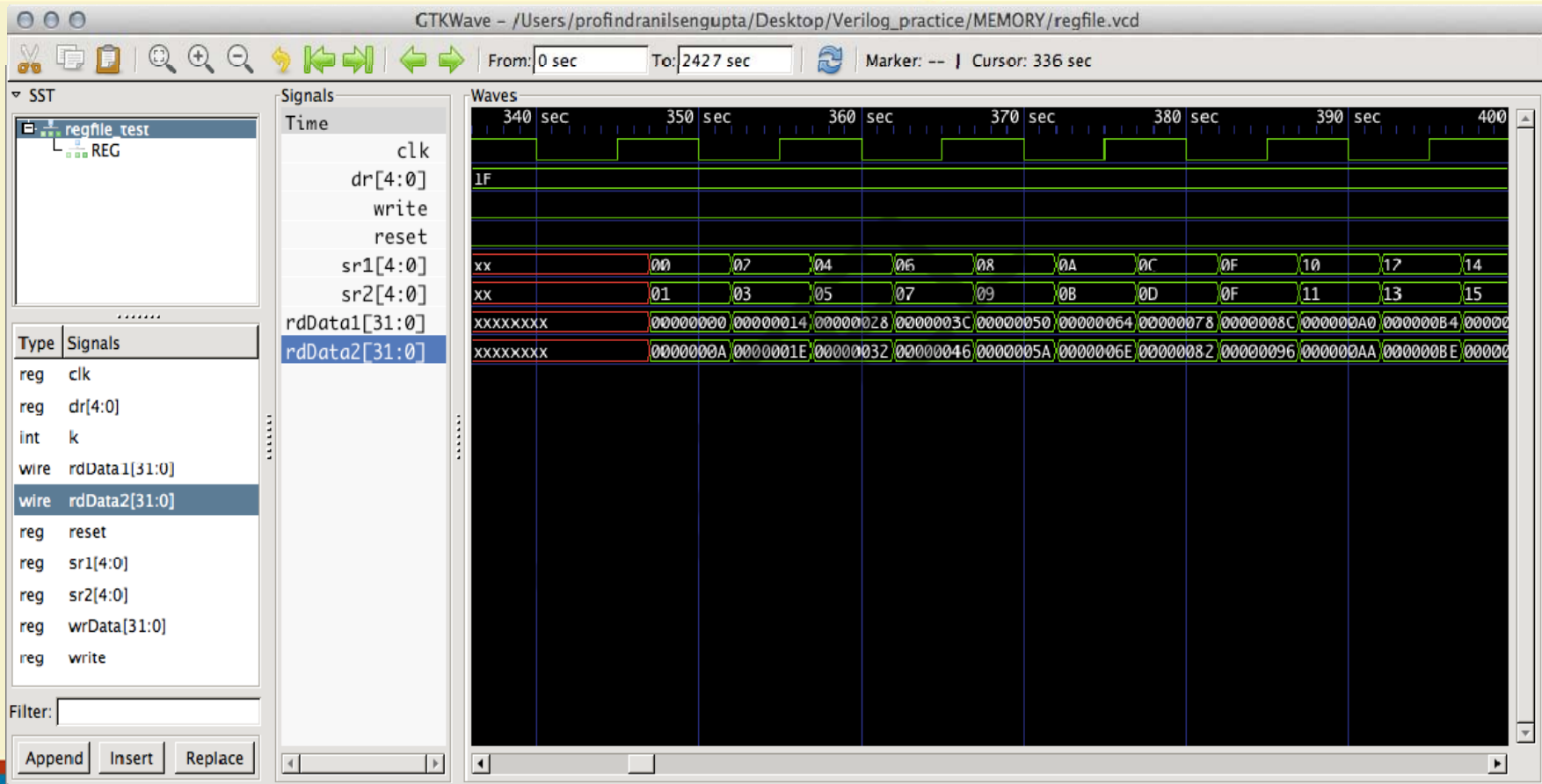

END OF LECTURE 31





IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 32: BASIC PIPELINING CONCEPTS

PROF. INDRANIL SENGUPTA

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

What is Pipelining?


- A mechanism for overlapped execution of several input sets by partitioning some computation into a set of k sub-computations (or stages).
 - Very nominal increase in the cost of implementation.
 - Very significant speedup (ideally, k).
- Where are pipelining used in a computer system?
 - Instruction execution: Several instructions executed in some sequence.
 - Arithmetic computation: Same operation carried out on several data sets.
 - Memory access: Several memory accesses to consecutive locations are made.



A Real-life Example

- Suppose you have built a machine M that can wash (W), dry (D), and iron (R) clothes, one cloth at a time.


– Total time required is T .

 

For N clothes, time $T_1 = N.T$

- As an alternative, we split the machine into three smaller machines M_W , M_D and M_R , which can perform the specific task only.

 
– Time required by each of the smaller machines is $T/3$ (say).



For N clothes, time $T_3 = (2 + N).T/3$



How does the pipeline work?

 

Finishing times:

- Cloth-1 – $3.T/3$
- Cloth-2 – $4.T/3$
- Cloth-3 – $5.T/3$
- ...
- Cloth-N – $(2 + N).T/3$




Extending the Concept to Processor Pipeline

- The same concept can be extended to hardware pipelines.
- Suppose we want to attain k times speedup for some computation.
 - **Alternative 1:** Replicate the hardware k times \rightarrow cost also goes up k times.
 - **Alternative 2:** Split the computation into k stages \rightarrow very nominal cost increase.
- Need for buffering:
 - In the washing example, we need a tray between machines (W & D, and D & R) to keep the cloth temporarily before it is accepted by the next machine.
 - Similarly in hardware pipeline, we need a *latch* between successive stages to hold the intermediate results temporarily.



Model of a Synchronous k-stage Pipeline

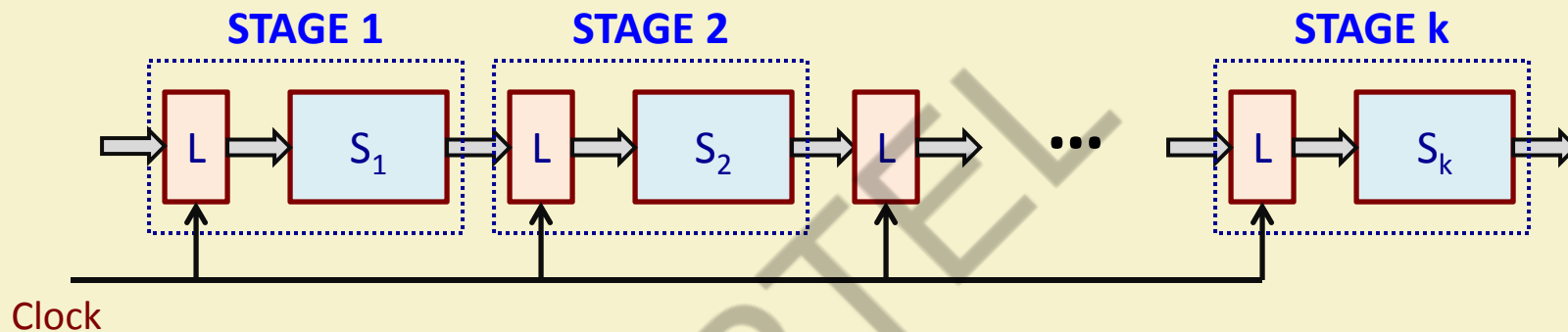


- The latches are made with master-slave flip-flops, and serve the purpose of isolating inputs from outputs.
- The pipeline stages are typically combinational circuits.
- When *Clock* is applied, all latches transfer data to the next stage simultaneously.



Structure of the Pipeline

 - **Linear Pipeline**: The stages that constitute the pipeline are executed one by one in sequence (say, from left to right).
- **Non-linear Pipeline**: The stages may not execute in a linear sequence (say, a stage may execute more than once for a given data set).




A possible sequence: A, B, C, B, C, A, C, A



Reservation Table

- The *Reservation Table* is a data structure that represents the utilization pattern of successive stages in a synchronous pipeline.
 - Basically a space-time diagram of the pipeline that shows precedence relationships among pipeline stages.
 - X-axis shows the time steps
 - Y-axis shows the stages
 - Number of columns give evaluation time.
 - The reservation table for a 4-stage linear pipeline is shown.

 

	1	2	3	4
S_1	X			
S_2		X		
S_3			X	
S_4				X




- Reservation table for a 3-stage dynamic multi-function pipeline is shown.

- Contains feedforward and feedback connections.
- Two functions X and Y.

- Some characteristics:

 - *Multiple X's in a row* :: repeated use of the same stage in different cycles.
- *Contiguous X's in a row* :: extended use of a stage over more than one cycles.
- *Multiple X's in a column* :: multiple stages are used in parallel during a clock cycle.



	1	2	3	4	5	6	7	8
S_1	X					X		X
S_2		X		X				
S_3			X		X		X	

	1	2	3	4	5	6
S_1	Y				Y	
S_2			Y			
S_3		Y		Y		Y



Speedup and Efficiency

Some notations:

τ :: clock period of the pipeline

t_i :: time delay of the circuitry in stage S_i

d_L :: delay of a latch

Maximum stage delay $\tau_m = \max \{t_i\}$

Thus, $\tau = \tau_m + d_L$

Pipeline frequency $f = 1 / \tau$

- If one result is expected to come out of the pipeline every clock cycle, f will represent the maximum throughput of the pipeline.



- The total time to process N data sets is given by

$$T_k = [(k - 1) + N].\tau$$

$(k - 1) \tau$ time required to fill the pipeline
1 result every τ time after that \rightarrow total $N.\tau$

- For an equivalent non-pipelined processor (i.e. one stage), the total time is

$$T_1 = N.k.\tau$$

(ignoring the latch overheads)

- Speedup of the k -stage pipeline over the equivalent non-pipelined processor:

$$S_k = \frac{T_1}{T_k} = \frac{N.k.\tau}{k.\tau + (N - 1).\tau} = \frac{N.k}{k + (N - 1)}$$

As $N \rightarrow \infty$, $S_k \rightarrow k$



- Pipeline efficiency:

- How close is the performance to its ideal value?


$$E_k = \frac{S_k}{k} = \frac{N}{k + (N - 1)}$$

- Pipeline throughput:

- Number of operations completed per unit time.
 
$$H_k = \frac{N}{T_k} = \frac{N}{[k + (N - 1)] \cdot \tau}$$





Clock Skew / Jitter / Setup time

- The minimum clock period of the pipeline must satisfy the inequality:

$$\tau \geq t_{\text{skew+jitter}} + t_{\text{logic+setup}}$$

- Definitions:
 - *Skew*: Maximum delay difference between the arrival of clock signals at the stage latches.
 - *Jitter*: Maximum delay difference between the arrival of clock signal at the same latch.
 - *Logic delay*: Maximum delay of the slowest stage in the pipeline.
 - *Setup time*: Minimum time a signal needs to be stable at the input of a latch before it can be captured.



END OF LECTURE 32





IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 33: PIPELINE MODELING (PART 1)


PROF. INDRANIL SENGUPTA


DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING


A Simple Example

- We consider the example of a very simple 3-stage pipeline.
 - Four N -bit unsigned integers A , B , C and D as inputs.
 - An N -bit unsigned integer F as output.
 - The following computations are carried out in the stages:
 - a) $S1$: $x1 = A + B$; $x2 = C - D$;
 - b) $S2$: $x3 = x1 + x2$;
 - c) $S3$: $F = x3 * D$;
 - Point to note:
 - Input D is used in $S1$ as well as $S3$.
 - So the value of D must be forwarded to $S2$ and then to $S3$.



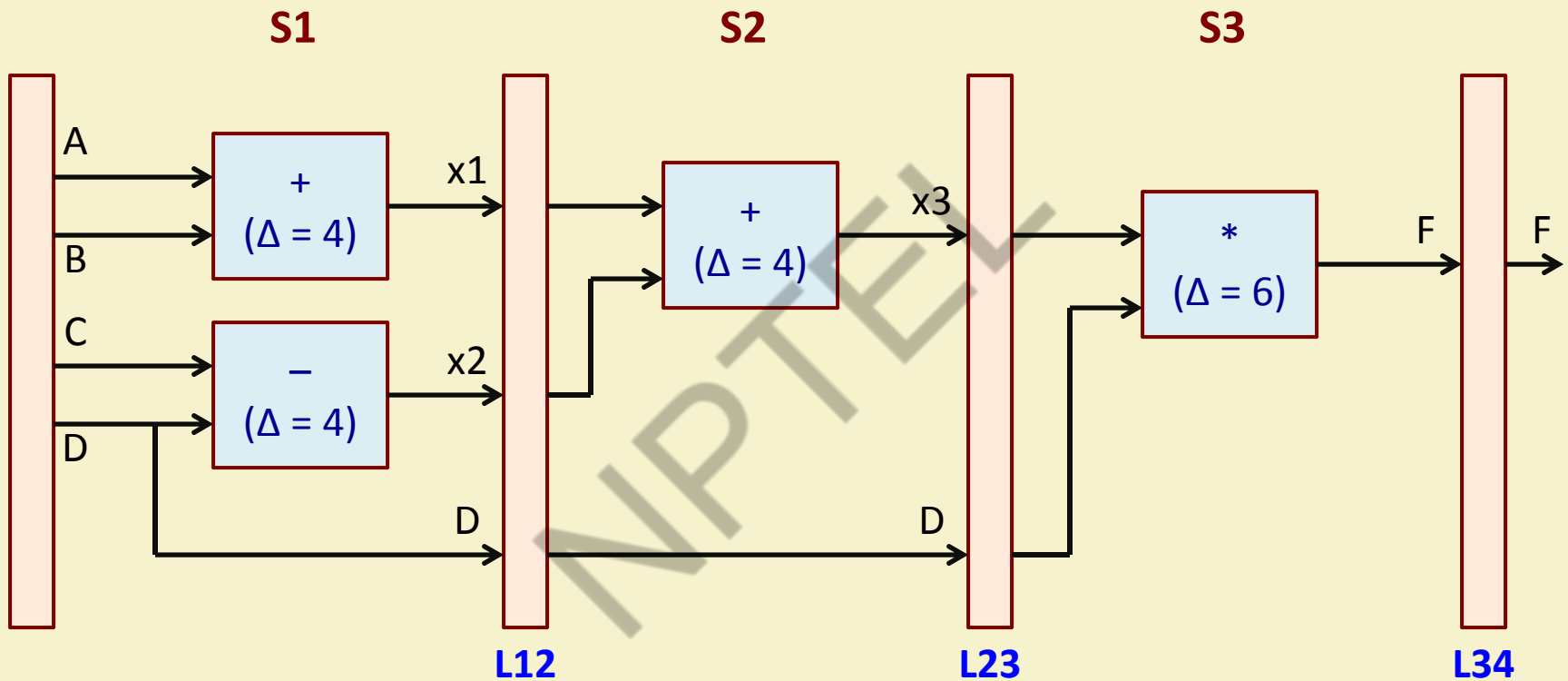

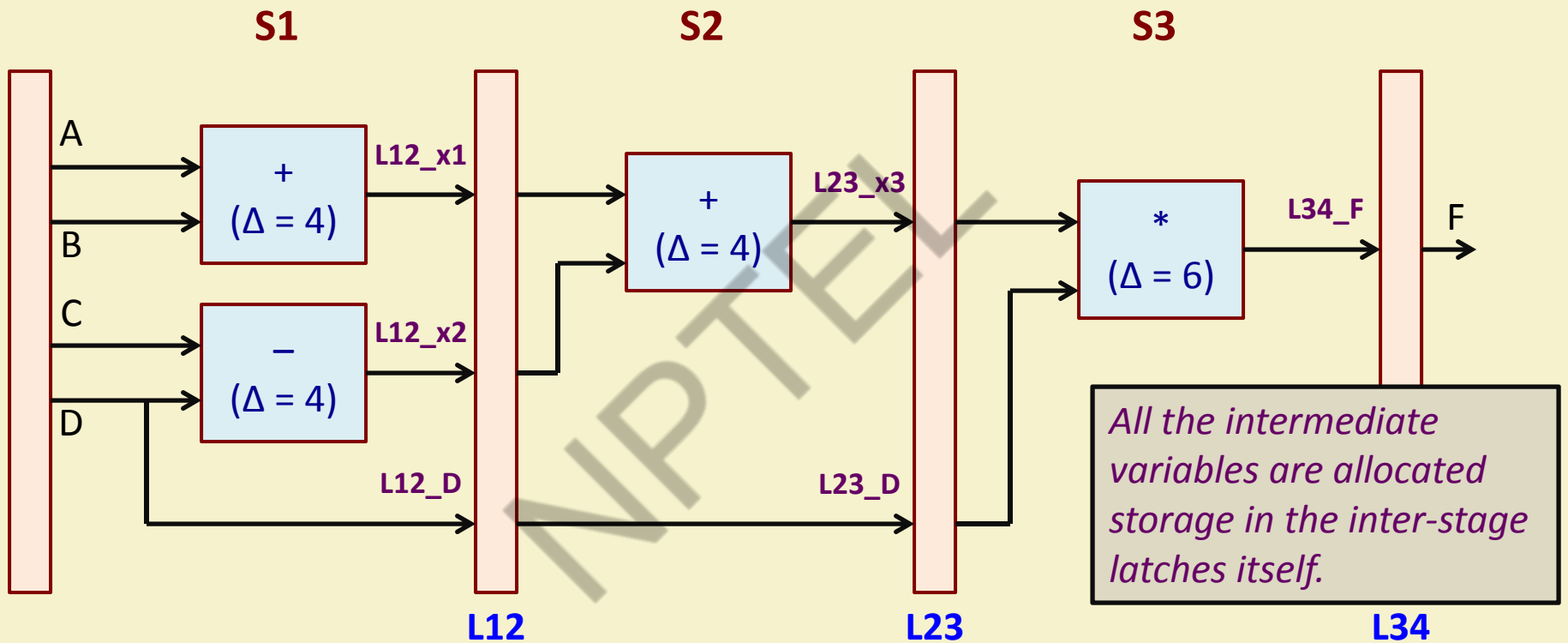

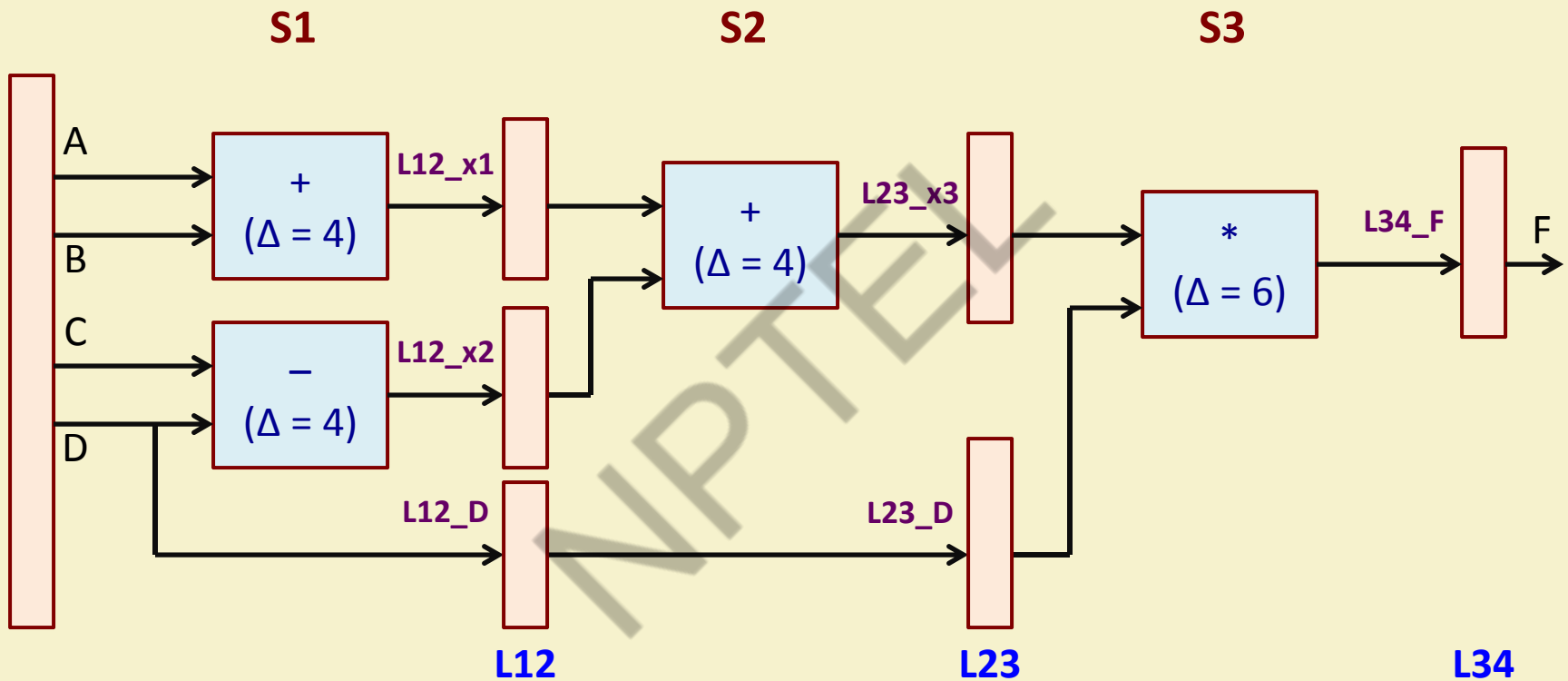

Pipeline Modeling

```
module pipe_ex (F, A, B, C, D, clk);  
    parameter N = 10;  
  
    input [N-1:0] A, B, C, D;  
    input clk;  
    output [N-1:0] F;  
    reg [N-1:0] L12_x1, L12_x2, L12_D, L23_x3, L23_D, L34_F;  
  
    assign F = L34_F;  
  
    always @(posedge clk)  
        begin  
            L12_x1 <= #4 A + B;  
            L12_x2 <= #4 C - D;  
            L12_D   <= D;                                // ** STAGE 1 **  
        end  
endmodule
```



```
L23_x3 <= #4 L12_x1 + L12_x2;  
L23_D  <= L12_D;           // ** STAGE 2 **  
  
L34_F  <= #6 L23_x3 * L23_D; // ** STAGE 3 **  
end  
  
endmodule
```



```

module pipe_ex (F, A, B, C, D, clk);
    parameter N = 10;

    input [N-1:0] A, B, C, D;
    input clk;
    output [N-1:0] F;
    reg [N-1:0] L12_x1, L12_x2, L12_D, L23_x3, L23_D, L34_F;

    assign F = L34_F;

    always @(posedge clk)                                // ** STAGE 1 **
    begin
        L12_x1 <= #4 A + B;
        L12_x2 <= #4 C - D;
        L12_D   <= D;
    end

```

Alternate way of coding:

- One stage per “always” block.
- Code is more readable.



```

always @(posedge clk)                                // ** STAGE 2 **
begin
    L23_x3 <= #4 L12_x1 + L12_x2;
    L23_D  <= L12_D;
end

always @(posedge clk)                                // ** STAGE 3 **
    L34_F  <= #6 L23_x3 * L23_D;

endmodule

```



Pipeline Test Bench

```
module pipel_test;

    parameter N = 10;
    wire [N-1:0] F;
    reg [N-1:0] A, B, C, D;
    reg clk;

    pipe_ex MYPIPE (F, A, B, C, D, clk);

    initial    clk = 0;

    always    #10 clk = ~clk;
```



```

initial
begin
    #5  A = 10; B = 12; C = 6;  D = 3;  // F = 75    (4Bh)
    #20 A = 10; B = 10; C = 5;  D = 3;  // F = 66    (42h)
    #20 A = 20; B = 11; C = 1;  D = 4;  // F = 112   (70h)
    #20 A = 15; B = 10; C = 8;  D = 2;  // F = 62    (3Eh)
    #20 A = 8;  B = 15; C = 5;  D = 0;  // F = 0      (00h)
    #20 A = 10; B = 20; C = 5;  D = 3;  // F = 66    (42h)
    #20 A = 10; B = 10; C = 30; D = 1;  // F = 49    (31h)
    #20 A = 30; B = 1;  C = 2;  D = 4;  // F = 116   (74h)
end

initial
begin
    $dumpfile ("pipe1.vcd");
    $dumpvars (0, pipe1_test);
    $monitor ("Time: %d, F = %d", $time, F);
    #300 $finish;
end
endmodule

```



```
Time:    0, F =    x
Time:   56, F =   75
Time:   76, F =   66
Time:   96, F =  112
Time:  116, F =   62
Time:  136, F =    0
Time:  156, F =   96
Time:  179, F =   49
Time:  196, F =  116
```



A Warning

- In this example, we have used a single phase clock to load all the inter-stage registers in the pipeline.
- In a real pipeline, this may lead to race condition.
- Possible solution:
 - Use master-phase flip-flops in the registers.
 - Use a two-phase clock to clock the alternate stages.
- We shall illustrate the two-phase clocking approach in the next example.



END OF LECTURE 33





IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 34: PIPELINE MODELING (PART 2)

PROF. INDRANIL SENGUPTA

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

A More Complex Example

- Consider a pipeline that carries out the following stage-wise operations:
 - *Inputs*: Three register addresses (*rs1*, *rs2* and *rd*), an ALU function (*func*), and a memory address (*addr*).
 - *Stage 1*: Read two 16-bit numbers from the registers specified by “*rs1*” and “*rs2*”, and store them in *A* and *B*.
 - *Stage 2*: Perform an ALU operation on *A* and *B* specified by “*func*”, and store it in *Z*.
 - *Stage 3*: Write the value of *Z* in the register specified by “*rd*”.
 - *Stage 4*: Also write the value of *Z* in memory location “*addr*”.



The Assumptions

- There is a register bank containing 16 16-bit registers.
 - 4-bits are required to specify a register address.
 - 2 register reads and 1 register write can be performed every clock cycle.
 - Register addresses are “*rs1*”, “*rs2*”, and “*rd*”.
- Assume that the memory is organized as *256 x 16*.
 - 8-bits are required to specify memory address.
 - Every memory location contains 16 bits of data, which can be read in a single clock cycle.
 - Memory address specified as “*addr*”.



- The ALU function is selected by a 4-bit field “*func*”, as follows:

0000: ADD

0001: SUB

0010: MUL

0011: SELA

0100: SELB

0101: AND

0110: OR

0111: XOR


1000: NEGA

1001: NEGB

1010: SRA


1011: SLA



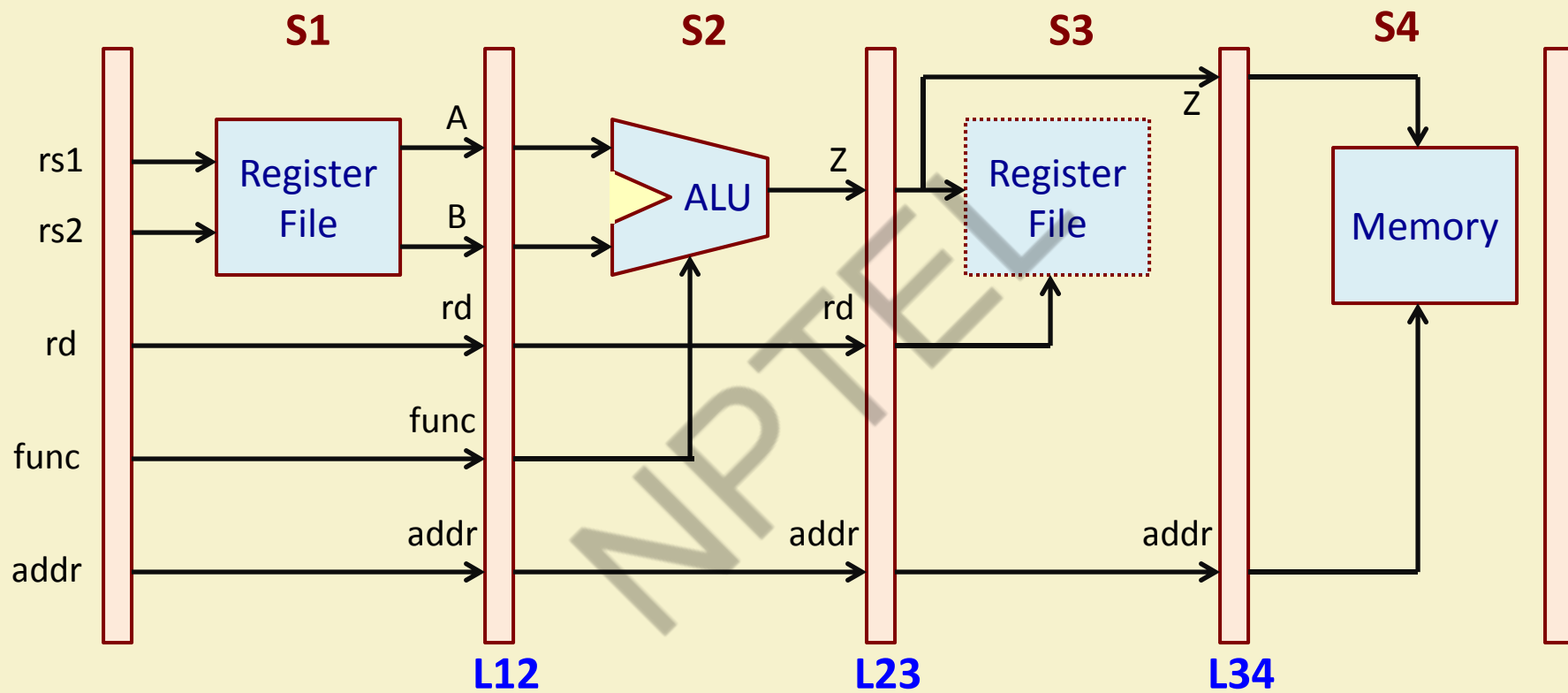

Clocking Issue in Pipeline

 - It is important that the consecutive stages be applied suitable clocks for correct operation.
- Two options:
 - a) Use master/slave flip-flops in the latches to avoid race condition.
 - b) Use non-overlapping two-phase clock for the consecutive pipeline stages.



```

module pipe_ex2 (Zout, rs1, rs2, rd, func, addr, clk1, clk2);

    input [3:0] rs1, rs2, rd, func;
    input [7:0] addr;
    input write, clk1, clk2;          // Two-phase clock
    output [15:0] Zout;

    reg [15:0] L12_A, L12_B, L23_Z, L34_Z;
    reg [3:0]  L12_rd, L12_func, L23_rd;
    reg [7:0]  L12_addr, L23_addr, L34_addr;

    reg [15:0] regbank [0:15];      // Register bank
    reg [15:0] mem [0:255];         // 256 x 16 memory

    assign Zout = L34_Z;

```

Pipeline Modeling



```
always @(posedge clk1)
begin
    L12_A      <= #2 regbank[rs1];
    L12_B      <= #2 regbank[rs2];
    L12_rd     <= #2 rd;
    L12_func    <= #2 func;
    L12_addr   <= #2 addr;           // ** STAGE 1 **
end
```



```

always @(negedge clk2)
begin
    case (func)
        0: L23_Z <= #2 L12_A + L12_B;
        1: L23_Z <= #2 L12_A - L12_B;
        2: L23_Z <= #2 L12_A * L12_B;
        3: L23_Z <= #2 L12_A;
        4: L23_Z <= #2 L12_B;
        5: L23_Z <= #2 L12_A & L12_B;
        6: L23_Z <= #2 L12_A | L12_B;
        7: L23_Z <= #2 L12_A ^ L12_B;
        8: L23_Z <= #2 ~ L12_A;
        9: L23_Z <= #2 ~ L12_B;
        10: L23_Z <= #2 L12_A >> 1;
        11: L23_Z <= #2 L12_A << 1;
        default: L23_Z <= #2 16'hxxxx;
    endcase
    L23_rd <= #2 L12_rd;
    L23_addr <= #2 L12_addr;
end

```

// ** STAGE 2 **



```

always @(posedge clk1)
begin
    regbank[L23_rd] <= #2 L23_Z;
    L34_Z          <= #2 L23_Z;
    L34_addr       <= #2 L23_addr;    // ** STAGE 3 **
end

always @(negedge clk2)
begin
    mem[L34_addr] <= #2 L34_Z;        // ** STAGE 4 **
end

endmodule

```



Pipeline Test Bench

```
module pipe2_test;

    wire [15:0] Z;
    reg [3:0] rs1, rs2, rd, func;
    reg [7:0] addr;
    reg clk1, clk2;
    integer k;

    pipe_ex2 MYPIPE (Z, rs1, rs2, rd, func, addr, clk1, clk2);

    initial
    begin
        clk1 = 0; clk2 = 0;
        repeat (20) // Generating two-phase clock
            begin
                #5 clk1 = 1; #5 clk1 = 0;
                #5 clk2 = 1; #5 clk2 = 0;
            end
        end

    initial
    for (k=0; k<16; k=k+1)
        MYPIPE.regbank[k] = k; // Initialize registers
```

```

initial
begin
    #5    rs1 = 3;  rs2 = 5;  rd = 10; func = 0;  addr = 125;  // ADD
    #20   rs1 = 3;  rs2 = 8;  rd = 12; func = 2;  addr = 126;  // MUL
    #20   rs1 = 10; rs2 = 5;  rd = 14; func = 1;  addr = 128;  // SUB
    #20   rs1 = 7;  rs2 = 3;  rd = 13; func = 11; addr = 127;  // SLA
    #20   rs1 = 10; rs2 = 5;  rd = 15; func = 1;  addr = 129;  // SUB
    #20   rs1 = 12; rs2 = 13; rd = 16; func = 0;  addr = 130;  // ADD

    #60 for (k=125; k<131; k=k+1)
        $display ("Mem[%3d] = %3d", k, MYPIPE.mem[k]);
    end

initial
begin
    $dumpfile ("pipe2.vcd");
    $dumpvars (0, pipe2_test);
    $monitor ("Time: %3d, F = %3d", $time, Z);
    #300 $finish;
end

endmodule


```



Simulation Results
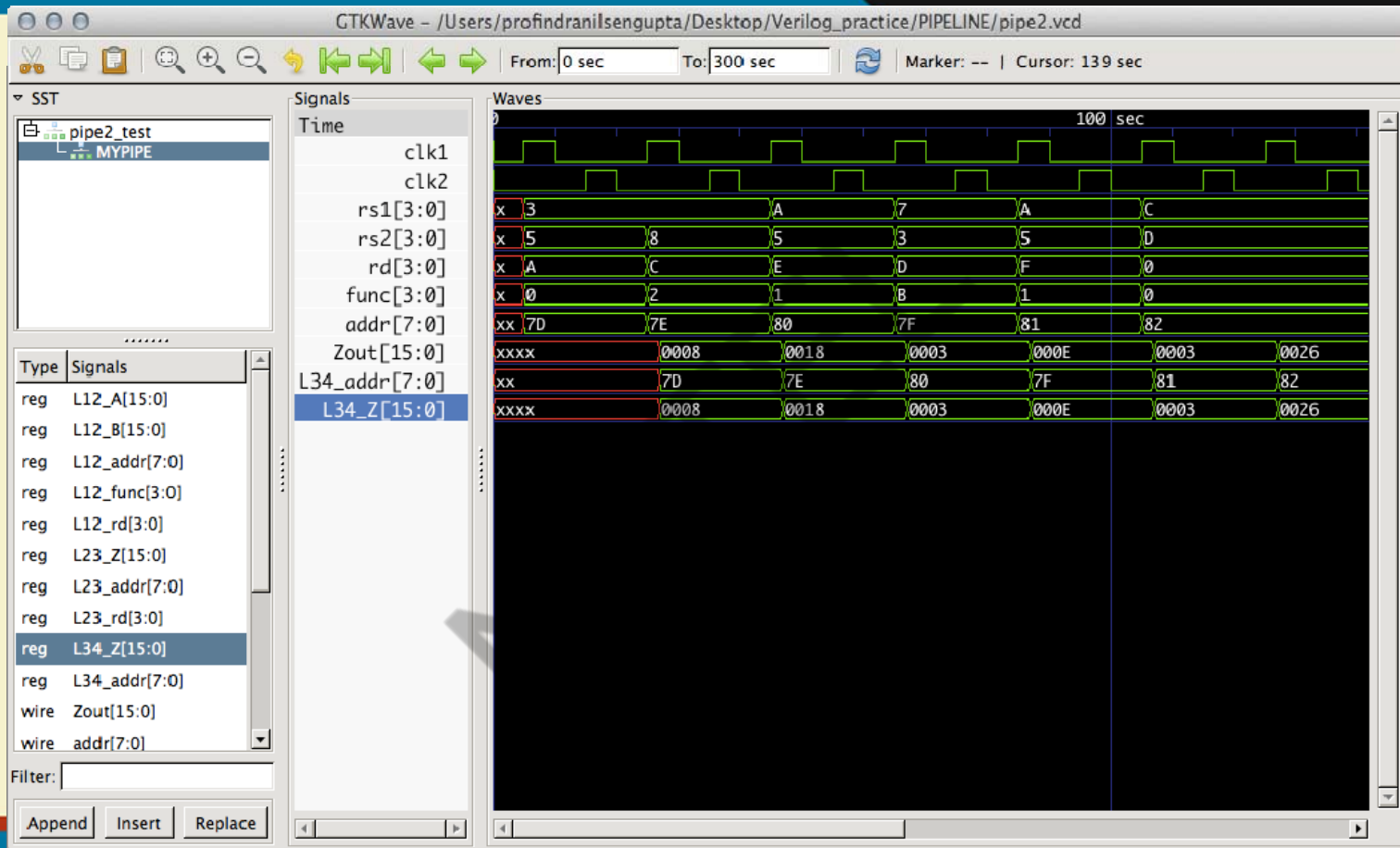
```
Time: 0, F = x
Time: 27, F = 8
Time: 47, F = 24
Time: 67, F = 3
Time: 87, F = 14
Time: 107, F = 3
Time: 127, F = 38
Mem[125] = 8
Mem[126] = 24
Mem[127] = 14
Mem[128] = 3
Mem[129] = 3
Mem[130] = 38
```





END OF LECTURE 34





IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 35: SWITCH LEVEL MODELING (PART 1)

PROF. INDRANIL SENGUPTA

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

Introduction

- A switch level circuit comprises of a netlist of MOS transistors.
- It is not very common for a designer to design modules using transistors.
 - May be required in very specific cases, for designing leaf-level modules in a hierarchical design.
- Verilog provides the ability to model digital circuits at the MOS transistor level.
 - Transistors function as switches; they either conduct (ON) or are open (OFF).
- The four logic levels 0, 1, X, Z and the associated signal drive strengths help in the modeling.
- Two types of switches supported: *ideal* or *resistive*.



Various Switch Primitives in Verilog

- Ideal MOS switches
 - nmos, pmos, cmos
- Resistive MOS switches
 - rnmos, rpmos, rcmos
- Ideal Bidirectional switches
 - tran, tranif0, tranif1
- Resistive Bidirectional switches
 - rtran, rtranif0, rtranif1
- Power and Ground nets
 - supply1, supply0
- Pullup and Pulldown
 - pullup, pulldown




(a) NMOS and PMOS Switches

- Declared with keywords “*nmos*” and “*pmos*”.
- Format for instantiation:

```
nmos (or pmos) [instance_name] (output, input, control);
```


Here, “instance_name” is optional.

Also called pass transistors.

 

nmos		control			
		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	z	z	z

(a) nMOS switch

 

pmos		control			
		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	z	z	z	z

(b) pMOS switch




(b) CMOS Switch (Transmission Gate)

- Declared with keywords “*cmos*”.


- Format for instantiation:

```
cmos [instance_name] (output, input, ncontrol, pcontrol);
```

Here also, “instance_name” is optional.

 


Example 1: CMOS Inverter

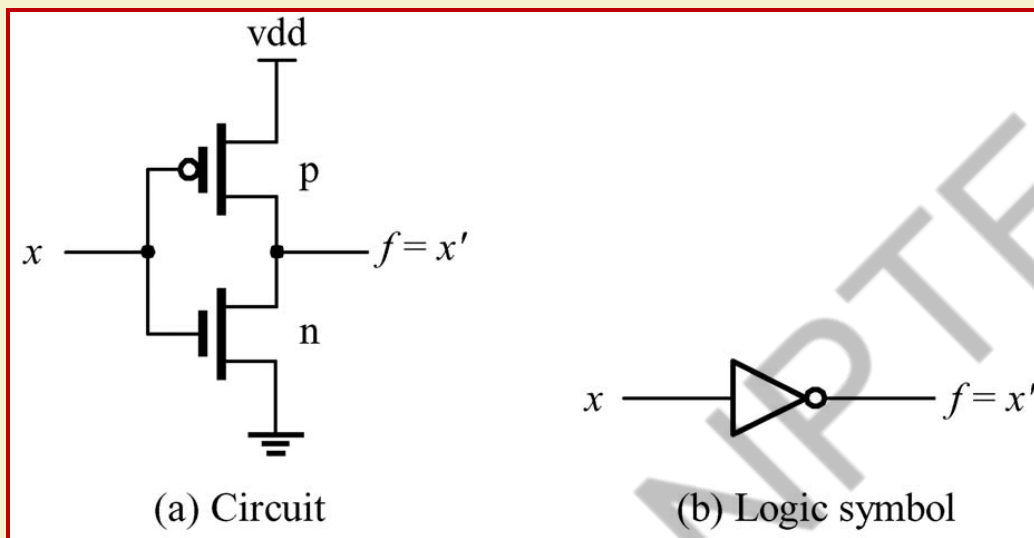

```
module cmosnot (x, f);  
  input x;  
  output f;  
  supply1 vdd;  
  supply0 gnd;  
  
  pmos p1 (f, vdd, x);  
  nmos n1 (f, gnd, x);  
  
endmodule
```



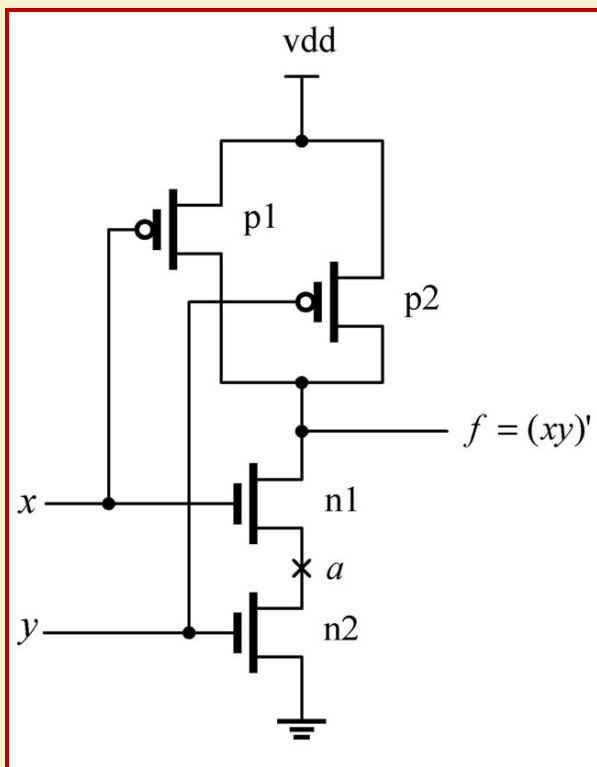

Example 2: CMOS NAND Gate

```
module cmosnand (x, y, f);
    input x, y;
    output f;
    supply1 vdd;
    supply0 gnd;
    wire a;

    pmos p1 (f, vdd, x);
    pmos p2 (f, vdd, y);
    nmos n1 (f, a, x);
    nmos n2 (a, gnd, y);

endmodule
```



```
module cmosnand_test;
```

```
    reg in1, in2;
```

```
    wire out;
```

```
    integer k;
```

```
    cmosnand MYNAND2 (in1, in2, out);
```

```
    initial
```

```
        begin
```

```
            for (k=0; k<4; k=k+1)
```

```
                begin
```

```
                    #5 {in1,in2} = k;
```

```
                    $display ("In1: %b, In2: %b, Out: %b", in1, in2,  
out);
```

```
                end
```

```
            end
```

```
endmodule
```

```
In1: 0, In2: 0, Out: 1
```


```
In1: 0, In2: 1, Out: 1
```

```
In1: 1, In2: 0, Out: 1
```

```
In1: 1, In2: 1, Out: 0
```



Example 3: Pseudo-NMOS NOR Gate

 

```
module pseudonor (x, y, f);  
  input x, y;  
  output f;  
  supply0 gnd;  
  nmos nx (f, gnd, x);  
  nmos ny (f, gnd, y);  
  pullup (f);  
endmodule
```



```
module pseudonor_test;
```

```
    reg in1, in2;
```

```
    wire out;
```

```
    integer k;
```

```
    pseudonor MYNOR2 (in1, in2, out);
```

```
    initial
```

```
        begin
```

```
            for (k=0; k<4; k=k+1)
```

```
                begin
```

```
                    #5 {in1,in2} = k;
```

```
                    $display ("In1: %b, In2: %b, Out: %b", in1, in2,  
out);
```

```
                end
```

```
            end
```

```
endmodule
```

```
In1: 0, In2: 0, Out: 1
```


```
In1: 0, In2: 1, Out: 0
```

```
In1: 1, In2: 0, Out: 0
```

```
In1: 1, In2: 1, Out: 0
```



Example 4: CMOS 2x1 Multiplexer

 

```
module mux_2to1 (out, s, i0, i1);  
    input s, i0, i1;  
    output out;  
    wire sbar;  
    not (sbar, s);  
    cmos cmos_a (out, i0, sbar, s);  
    cmos cmos_b (out, i1, s, sbar);  
endmodule
```



```

module cmosmux_test;

  reg sel, in0, in1;
  wire out;
  integer k;

  cmosmux MUX21 (out, sel, in0, in1);

  initial
    begin
      for (k=0; k<8; k=k+1)
        begin
          #5 {sel,in0,in1} = k;
          $display ("Sel: %b, In0: %b, In1: %b, Out: %b",
                    sel, in0, in1,
                    out);
        end
      end
    end
endmodule


```

Sel: 0, In0: 0, In1: 0, Out: 0
Sel: 0, In0: 0, In1: 1, Out: 0
Sel: 0, In0: 1, In1: 0, Out: 1
Sel: 0, In0: 1, In1: 1, Out: 1
Sel: 1, In0: 0, In1: 0, Out: 0
Sel: 1, In0: 0, In1: 1, Out: 1
Sel: 1, In0: 1, In1: 0, Out: 0
Sel: 1, In0: 1, In1: 1, Out: 1



 (c) Bidirectional Switches

- “*nmos*”, “*pmos*”, and “*cmos*” gates conduct in one direction (drain to source).
- When it is required for devices to conduct in both direction, we use bidirectional switches.
- Three types of bidirectional switches: “*tran*”, “*tranif0*”, and “*tranif1*”.



Syntax:

```
tran      [instance_name] (inout1, inout2);  
tranif0   [instance_name] (inout1, inout2, cnt1);  
tranif1   [instance_name] (inout1, inout2, cnt1);
```



END OF LECTURE 35





IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 36: SWITCH LEVEL MODELING (PART 2)


PROF. INDRANIL SENGUPTA

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

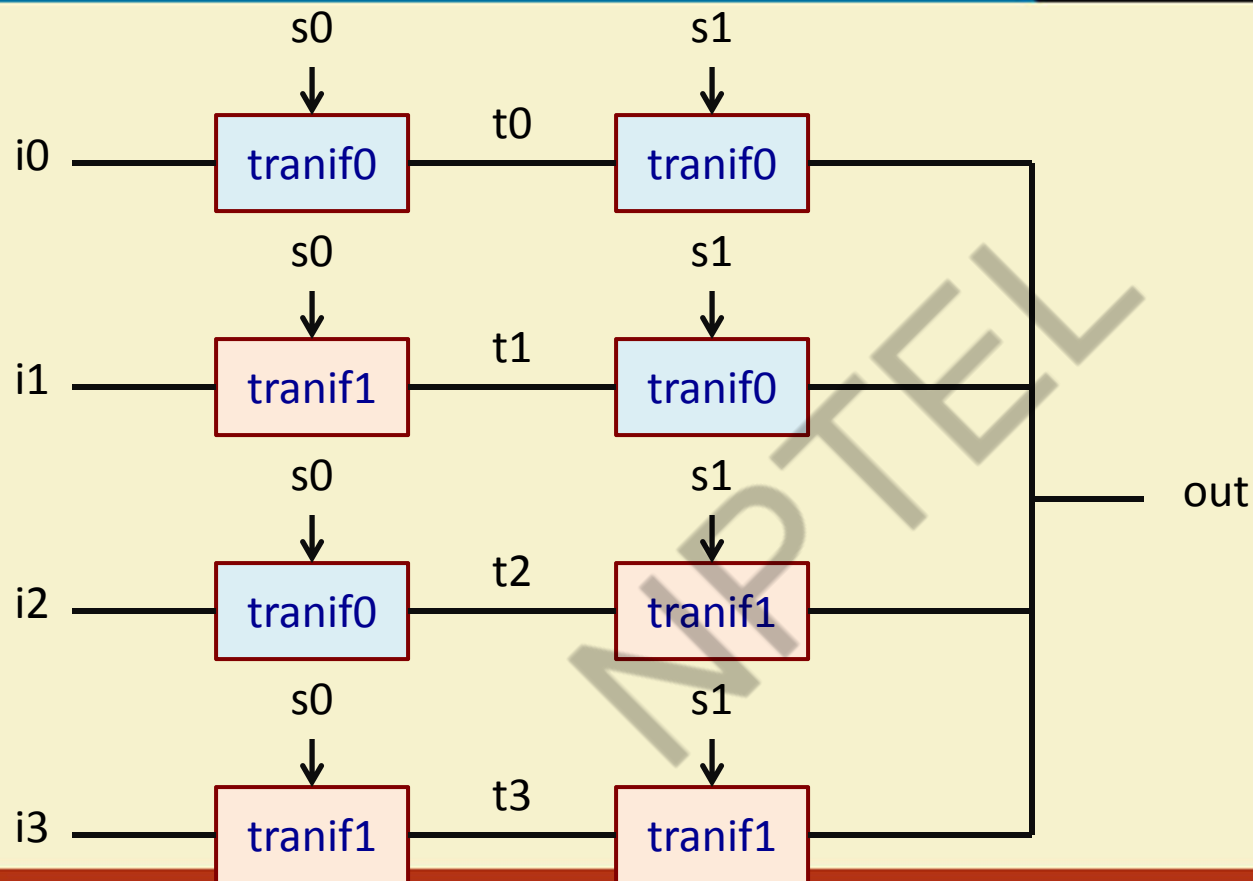Example 5: CMOS 4x1 Multiplexer using “tran” Switches

```
module mux_4to1 (out, s0, s1, i0, i1, i2, i3);  
    input s0, s1, i0, i1, i2, i3;  
    output out;  
    wire t0, t1, t2, t3;  
  
    tranif0 (i0, t0, s0);    tranif0 (t0, out, s1);  
    tranif1 (i1, t1, s0);    tranif0 (t1, out, s1);  
    tranif0 (i2, t2, s0);    tranif1 (t2, out, s1);  
    tranif1 (i3, t3, s0);    tranif1 (t3, out, s1);  
endmodule
```





**Schematic
Diagram**



Test Bench

```
module mux41_test;
    reg s0, s1, i0, i1, i2, i3;
    wire out;
    integer k;
    mux_4to1 MYMUX41 (out, s0, s1, i0, i1, i2, i3);
    initial
        begin
            for (k=0; k<64; k=k+1)
                begin
                    #5 {s0,s1,i0,i1,i2,i3} = k;
                    $display ("Sel: %2b, In: %4b, Out: %b",
                               {s0,s1}, {i0,i1,i2,i3}, out);
                end
            end
        end
    endmodule
```



Simulation Results

```
Sel: 00, In: 0000, Out: x
Sel: 00, In: 0001, Out: 0
Sel: 00, In: 0010, Out: 0
Sel: 00, In: 0011, Out: 0
Sel: 00, In: 0100, Out: 0
Sel: 00, In: 0101, Out: 0
Sel: 00, In: 0110, Out: 0
Sel: 00, In: 0111, Out: 0
Sel: 00, In: 1000, Out: 0
Sel: 00, In: 1001, Out: 1
Sel: 00, In: 1010, Out: 1
Sel: 00, In: 1011, Out: 1
Sel: 00, In: 1100, Out: 1
Sel: 00, In: 1101, Out: 1
Sel: 00, In: 1110, Out: 1
Sel: 00, In: 1111, Out: 1
```

```
Sel: 01, In: 0000, Out: 1
Sel: 01, In: 0001, Out: 0
Sel: 01, In: 0010, Out: 0
Sel: 01, In: 0011, Out: 1
Sel: 01, In: 0100, Out: 1
Sel: 01, In: 0101, Out: 0
Sel: 01, In: 0110, Out: 0
Sel: 01, In: 0111, Out: 1
Sel: 01, In: 1000, Out: 1
Sel: 01, In: 1001, Out: 0
Sel: 01, In: 1010, Out: 0
Sel: 01, In: 1011, Out: 1
Sel: 01, In: 1100, Out: 1
Sel: 01, In: 1101, Out: 0
Sel: 01, In: 1110, Out: 0
Sel: 01, In: 1111, Out: 1
```



Simulation Results

```
Sel: 10, In: 0000, Out: 1
Sel: 10, In: 0001, Out: 0
Sel: 10, In: 0010, Out: 0
Sel: 10, In: 0011, Out: 0
Sel: 10, In: 0100, Out: 0
Sel: 10, In: 0101, Out: 1
Sel: 10, In: 0110, Out: 1
Sel: 10, In: 0111, Out: 1
Sel: 10, In: 1000, Out: 1
Sel: 10, In: 1001, Out: 0
Sel: 10, In: 1010, Out: 0
Sel: 10, In: 1011, Out: 0
Sel: 10, In: 1100, Out: 0
Sel: 10, In: 1101, Out: 1
Sel: 10, In: 1110, Out: 1
Sel: 10, In: 1111, Out: 1
```

```
Sel: 11, In: 0000, Out: 1
Sel: 11, In: 0001, Out: 0
Sel: 11, In: 0010, Out: 1
Sel: 11, In: 0011, Out: 0
Sel: 11, In: 0100, Out: 1
Sel: 11, In: 0101, Out: 0
Sel: 11, In: 0110, Out: 1
Sel: 11, In: 0111, Out: 0
Sel: 11, In: 1000, Out: 1
Sel: 11, In: 1001, Out: 0
Sel: 11, In: 1010, Out: 1
Sel: 11, In: 1011, Out: 0
Sel: 11, In: 1100, Out: 1
Sel: 11, In: 1101, Out: 0
Sel: 11, In: 1110, Out: 1
Sel: 11, In: 1111, Out: 0
```



Example 6: Full Adder using Transistor Level Modeling

```
module fulladder (sum, cout, a, b, cin);  
    input a, b, cin;  
    output sum, cout;  
    fa_sum SUM (sum, a, b, cin);  
    fa_carry CARRY (cout, a, b, cin);  
endmodule
```

```
module fa_carry (cout, a, b, cin);  
    input a, b, cin;  
    output cout;  
    wire t1, t2, t3, t4, t5;  
    cmosnand N1 (t1, a, b);  
    cmosnand N2 (t2, a, cin);  
    cmosnand N3 (t3, b, cin);  
    cmosnand N4 (t4, t1, t2);  
    cmosnand N5 (t5, t4, t4);  
    cmosnand N6 (cout, t5, t3);  
endmodule
```



```

module myxor2 (out, a, b);
    input a, b;
    output out;
    wire t1, t2, t3, t4;

    cmosnand N1 (t1, a, a);
    cmosnand N2 (t2, b, b);
    cmosnand N3 (t3, a, t2);
    cmosnand N4 (t4, b, t1);
    cmosnand N5 (out, t3, t4);
endmodule

```

```

module fa_sum (sum, a, b, cin);
    input a, b, cin;
    output sum;
    wire t1, t2;

    myxor2 X1 (t1, a, b);
    myxor2 X2 (sum, t1, cin);
endmodule

```




```
module cmosnand (f, x, y);  
    input x, y;  
    output f;  
    supply1 vdd;  
    supply0 gnd;  
  
    pmos p1 (f, vdd, x);  
    pmos p2 (f, vdd, y);  
    nmos n1 (f, a, x);  
    nmos n2 (a, gnd, y);  
endmodule
```



Test Bench

```
module fulladder_test;

    reg a, b, cin;
    wire sum, cout;
    integer k;
    fulladder FA (sum, cout, a, b, cin);
    initial
        begin
            for (k=0; k<8; k=k+1)
                begin
                    #5 {a, b, cin} = k;
                    $display ("Inputs: %3b Sum: %b, Carry: %b",
                                {a,b,cin}, sum, cout);
                end
            end
        end
    endmodule
```



Simulation Results

Inputs: 000	Sum: 0,	Carry: 0
Inputs: 001	Sum: 1,	Carry: 0
Inputs: 010	Sum: 1,	Carry: 0
Inputs: 011	Sum: 0,	Carry: 1
Inputs: 100	Sum: 1,	Carry: 0
Inputs: 101	Sum: 0,	Carry: 1
Inputs: 110	Sum: 0,	Carry: 1
Inputs: 111	Sum: 1,	Carry: 1



Data Values and Signal Strengths

- Verilog supports 4 value levels and 8 strength levels to model the functionality of real hardware.
 - Strength levels are typically used to resolve conflicts between signal drivers of different strengths in real circuits.

Value Level	Represents
0	Logic 0 state
1	Logic 1 state
x	Unknown logic state
z	High impedance state

Initialization:

- All unconnected nets are set to “z”.
- All register variables set to “x”.



Strength	Type
supply	Driving
strong	Driving
pull	Driving
large	Storage
weak	Driving
medium	Storage
small	Storage
highz	High impedance

Strength increases ↑

- If two signals of unequal strengths get driven on a wire, the stronger signal will prevail.
- These are particularly useful for MOS level circuits, e.g. dynamic MOS.
- When a signal passes through a resistive switch, for example, its strength reduces.
- There is a convention followed for signal strength computation in MOS level circuits.
 - Details not discussed here.



Point to Note

- Most of the synthesis tools do not support switch level modeling.
 - Because it uses technology mapping from a given library.
 - Common gates and simple functional blocks are present in the library.
 - Thus it is not required to specify circuits at the transistor level.



END OF LECTURE 36



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

15