





NPTEL



Lecture 06: VERILOG LANGUAGE FEATURES (PART 1)

PROF. INDRANIL SENGUPTA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

Concept of Verilog "Module"

- In Verilog, the basic unit of hardware is called a **module**.
 - A module cannot contain definition of other modules.
 - A module can, however, be **instantiated** within another module.
 - Instantiation allows the creation of a **hierarchy** in Verilog description.

```
module module_name (list_of_ports);
  input/output declarations
  local net declarations
  Parallel statements
endmodule
```

Hardware Modeling Using Verilog

```
// A simple AND function
module simpleand (f, x, y);
  input x, y;
  output f;
  assign f = x & y;
endmodule
```


This is a behavioral description. The synthesis tool will decide how the realize f:

- Using a single AND gate
- Using a NAND gate followed by a NOT gate.

```
/* A 2-level combinational circuit */
module two_level (a, b, c, d, f);
  input a, b, c, d;
  output f;
  wire t1, t2; // Intermediate lines
  assign t1 = a & b;
  assign t2 = ~(c | d);
  assign f = ~(t1 & t2);
endmodule
```

This is also behavioral description.

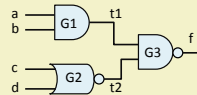- One possible gate level realization is shown.
- t1 and t2 are intermediate lines; termed as wire data type.



- Point to note:
 - The "assign" statement represents continuous assignment, whereby the variable on the LHS gets updated whenever the expression on the RHS changes.


```
assign variable = expression;
```
 - The LHS must be a "net" type variable, typically a "wire".
 - The RHS can contain both "register" and "net" type variables.
 - A Verilog module can contain any number of "assign" statements; they are typically placed in the beginning after the port declarations.
 - The "assign" statement models behavioral design style, and is typically used to model combinational circuits.

Data Types in Verilog

- A variable in Verilog belongs to one of two data types:
 - Net**
 - Must be continuously driven.
 - Cannot be used to store a value.
 - Used to model connections between continuous assignments and instantiations.
 - Register**
 - Retains the last value assigned to it.
 - Often used to represent storage elements, but sometimes it can translate to combinational circuits also.

(a) Net data type

- Nets represents connection between hardware elements.
- Nets are continuously driven by the outputs of the devices they are connected to.
 - Net "a" is continuously driven by the output of the AND gate.
- Nets are 1-bit values by default unless they are declared explicitly as vectors.
 - Default value of a net is "z".



- Various "Net" data types are supported for synthesis in Verilog:
 - wire, wor, wand, tri, supply0, supply1, etc.
- "wire" and "tri" are equivalent; when there are multiple drivers driving them, the driver outputs are shorted together.
- "wor" and "wand" inserts an OR and AND gate respectively at the connection.
- "supply0" and "supply1" model power supply connections.
- The Net data type "wire" is most common.

```

module use_wire (A, B, C, D, f);
  input  A, B, C, D;
  output f;
  wire  f;
  // net f declared as 'wire'

  assign f = A & B;
  assign f = C | D;
endmodule

```

For A = B = 1, and C = D = 0,
f will be indeterminate.

```

module use_wand (A, B, C, D, f);
  input  A, B, C, D;
  output f;
  wand  f;
  // net f declared as 'wand'

  assign f = A & B;
  assign f = C | D;
endmodule

```

Here, function realized will be
 $f = (A \& B) \& (C | D)$

```

module using_supply_wire (A, B, C, f);
  input  A, B, C;
  output f;
  supply0 gnd;
  supply1 vdd;
  nand G1 (t1, vdd, A, B);
  xor G2 (t2, C, gnd);
  and G3 (f, t1, t2);
endmodule

```

supply0 and supply1 have
the greatest signal
strength.

Data Values and Signal Strengths

- Verilog supports 4 value levels and 8 strength levels to model the functionality of real hardware.
 - Strength levels are typically used to resolve conflicts between signal drivers of different strengths in real circuits.

Value Level	Represents
0	Logic 0 state
1	Logic 1 state
x	Unknown logic state
z	High impedance state

Initialization:

- All unconnected nets are set to "z".
- All register variables set to "x".

Strength	Type
supply	Driving
strong	Driving
pull	Driving
large	Storage
weak	Driving
medium	Storage
small	Storage
highz	High impedance

Strength increases

- If two signals of unequal strengths get driven on a wire, the stronger signal will prevail.
- These are particularly useful for MOS level circuits, e.g. dynamic MOS.

END OF LECTURE 06

Lecture 07: VERILOG LANGUAGE FEATURES (PART 2)

PROF. INDRANIL SENGUPTA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

(b) Register Data Type

- In Verilog, a *“register”* is a variable that can *hold* a value.
 - Unlike a *“net”* that is continuously driven and cannot hold any value.
 - Does not necessarily mean that it will map to a hardware register during synthesis.
 - Combinational circuit specifications can also use register type variables.
- Register data types supported by Verilog:
 - reg* : Most widely used
 - integer* : Used for loop counting (typical use)
 - real* : Used to store floating-point numbers
 - time* : Keeps track of simulation time (not used in synthesis)

- “reg”* data type:
 - Default value of a *“reg”* data type is *“x”*.
 - It can be assigned a value in synchronism with a clock or even otherwise.
 - The declaration explicitly specifies the size (default is 1-bit):


```
reg x, y;           // Single-bit register variables
reg [15:0] bus;     // A 16-bit bus
```
 - Treated as an unsigned number in arithmetic expressions.
 - Must be used when we model actual sequential hardware elements like counters, shift registers, etc.

```
module simple_counter (clk, rst, count);
  input  clk, rst;
  output [31:0] count;
  reg [31:0] count;

  always @(posedge clk)
  begin
    if (rst)
      count = 32'b0;
    else
      count = count + 1;
  end
endmodule
```

32-bit counter with synchronous reset.

- Count value increases at the positive edge of the clock.
- If *“rst”* is high, the counter is reset at the positive edge of the next clock.

```
module simple_counter (clk, rst, count);
  input  clk, rst;
  output [31:0] count;
  reg [31:0] count;

  always @(posedge clk or posedge rst)
  begin
    if (rst)
      count = 32'b0;
    else
      count = count + 1;
  end
endmodule
```

32-bit counter with asynchronous reset.

- Here reset occurs whenever *“rst”* goes high.
- Does not synchronize with clock.

- **"integer"** data type:

- It is a general-purpose register data type used for manipulating quantities.
- More convenient to use in situations like loop counting than **"reg"**.
- It is treated as a 2's complement signed integer in arithmetic expressions.
- Default size is 32 bits; however, the synthesis tool tries to determine the size using data flow analysis.

- Example:

```
wire [15:0] X, Y;
integer C;
Z = X + Y;
```

- Size of Z can be deduced to be 17 (16 bits plus a carry).

- **"real"** data type:

- Used to store floating-point numbers.
- When a real value is assigned to an integer, the real number is rounded off to the nearest integer.

- Example:

```
real e, pi;
integer x;
initial
begin
    e = 2.718;          x = pi; // Gets value 3
    pi = 314.159e-2;
end
```

- **"time"** data type:

- In Verilog, simulation is carried out with respect to a logical clock called simulation time.
- The **"time"** data type can be used to store simulation time.
- The system function **"\$time"** gives the current simulation time.

- Example:

```
time curr_time;
initial
...
curr_time = $time;
```

Vectors

- Nets or **"reg"** type variable can be declared as vectors, of multiple bit widths.
 - If bit width is not specified, default size is 1-bit.
- Vectors are declared by specifying a range [**range1:range2**], where **range1** is always the most significant bit and **range2** is the least significant bit.

- Examples:

```
wire x, y, z;           // Single bit variables
wire [7:0] sum;         // MSB is sum[7], LSB is sum[0]
reg [31:0] MDR;
reg [1:10] data;        // MSB is data[1], LSB is data[10]
reg clock;
```

- Parts of a vector can be addressed and used in an expression.

- Example:

- A 32-bit instruction register, that contains a 6-bit opcode, three register operands of 5 bits each, and an 11-bit offset.

```
reg [31:0] IR;           opcode = IR[31:26];
reg [5:0] opcode;        reg1 = IR[25:21];
reg [4:0] reg1, reg2, reg3; reg2 = IR[20:16];
reg [10:0] offset;       reg3 = IR[15:11];
                        offset = IR[10:0];
```

Multi-dimensional Arrays and Memories

- Multi-dimensional arrays of any dimension can be declared in Verilog.

- Example:

```
reg [31:0] register_bank[15:0]; // 16 32-bit registers
integer matrix[7:0][15:0];
```

- Memories can be modeled in Verilog as a 1-D array of registers.

- Each element of the array is addressed by a single array index.

- Examples:

```
reg mem_bit[0:2047];      // 2K 1-bit words
reg [15:0] mem_word[0:1023]; // 1K 16-bit words
```

Specifying Constant Values

- A constant value may be specified in either the *sized* or the *unsized* form.

– Syntax of sized form:

`<size>'<base><number>`

– Examples:

```
4'b0101      // 4-bit binary number 0101
1'b0         // Logic 0 (1-bit)
12'hB3C      // 12-bit number 1011 0011 1100
12'h8xF      // 12-bit number 1000 xxxx 1111
25           // signed number, in 32 bits (size not specified)
```

Variables of type integer and real are typically expressed in unsized form.

Parameters

- A parameter is a constant with a given name.
 - We cannot specify the size of a parameter.
 - The size gets decided from the constant value itself; if size is not specified, it is taken to be 32 bits.
- Examples:


```
parameter HI = 25, LO = 5;
parameter up = 2b'00, down = 2b'01, steady = 2b'10;
parameter RED = 3b'100, YELLOW = 3b'010, GREEN = 3b'001;
```

```
// Parameterized design:: an N-bit counter
module counter (clear, clock, count);
  parameter N = 7;
  input clear, clock;
  output [0:N] count; reg [0:N] count;

  always @ (negedge clock)
    if (clear)
      count <= 0;
    else
      count <= count + 1;
endmodule
```

Any variable assigned within the "always" block must be of type "reg".

END OF LECTURE 07

Lecture 08: VERILOG LANGUAGE FEATURES (PART 3)

PROF. INDRANIL SENGUPTA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

Predefined Logic Gates in Verilog

- Verilog provides a set of predefined logic gates.
 - Can be instantiated within a module to create a structured design.
 - The gates respond to logic values (0, 1, x or z) in a logical way.

2-input AND

```
0 & 0 = 0
0 & 1 = 0
1 & 1 = 1
1 & x = x
0 & x = 0
1 & z = x
z & x = x
```

2-input OR

```
0 | 0 = 0
0 | 1 = 1
1 | 1 = 1
1 | x = x
0 | x = x
1 | z = x
z | x = x
```

2-input EXOR

```
0 ^ 0 = 0
0 ^ 1 = 1
1 ^ 1 = 0
1 ^ x = x
0 ^ x = x
1 ^ z = x
z ^ x = x
```

List of Primitive Gates

```

and G (out, in1, in2);    bufif1 G (out, in, ctrl);
nand G (out, in1, in2);   bufif0 G (out, in, ctrl);
or G (out, in1, in2);     notif0 G (out, in, ctrl);
nor G (out, in1, in2);    notif1 G (out, in, ctrl);
xor G (out, in1, in2);
xnor G (out, in1, in2);
not G (out, in);
buf G (out, in);

```

There are gates with tristate controls



Hardware Modeling Using Verilog

31

Some restriction when instantiating primitive gates:

- The output port must be connected to a net (e.g. a wire).
 - An "output" signal is a wire by default, unless explicitly declared as a register.
- The input ports may be connected to nets or register type variables.
- They have a single output but can have any number of inputs (except NOT and BUF).
- When instantiating a gate, an optional delay may be specified.
 - Used for simulation.
 - Logic synthesis tools ignore the time delays.




Hardware Modeling Using Verilog

32

```

`timescale 10ns/1ns
module exclusive_or (f, a, b);
  input a, b;
  output f;
  wire t1, t2, t3;
  nand #5 m1 (t1, a, b);
  and #5 m2 (t2, a, t1);
  and #5 m3 (t3, t1, b);
  nor #5 m4 (f, t2, t3);
endmodule

```

 

Hardware Modeling Using Verilog

33

The `timescale Directive

- Often in a single simulation, delay values in one module need to be specified in terms of some time unit, while those in some other module need to be specified in terms of some other time unit.
- The `timescale compiler directive can be used:


```
`timescale <reference_time_unit> / <time_precision>
```
- The <reference_time_unit> specifies the unit of measurement for time.
- The <time_precision> specifies the precision to which the delays are rounded off during simulation.
 - Valid values for specifying time unit and time precision are 1, 10 and 100.



Hardware Modeling Using Verilog

34

Example:

- ```
`timescale 10ns/1ns
```
- Reference time unit is 10ns, and simulation precision is 1ns.
  - If we specify #5 as delay, it will mean 50ns.
  - The time units can be specified in s (second), ms (millisecond), us (microsecond), ps (picosecond), and fs (femtosecond).



Hardware Modeling Using Verilog

35

### Specifying Connectivity during Instantiation

- When a module is instantiated within another module, there are two ways to specify the connectivity of the signal lines between the two modules.
  - Positional association
    - The parameters of the module being instantiated are listed in the same order as in the original module description.
  - Explicit association
    - The parameters of the module being instantiated are listed in arbitrary order.
    - Chance of errors is less.



Hardware Modeling Using Verilog

36

|                                                                                                                                                                                                                                                                                                                                          |                                                                                                                                                                                                     |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre> module testbench; reg X1,X2,X3,X4,X5,X6; wire OUT; example DUT(X1,X2,X3,X4,X5,X6,OUT);  initial begin \$monitor (\$time," X1=%b, X2=%b, X3=%b, X4=%b, X5=%b, X6=%b, OUT=%b", X1,X2,X3,X4,X5,X6,OUT); #5 X1=1;X2=0; X3=0; X4=1; X5=0; X6=0; #5 X1=0; X3=1; #5 X1=1; X3=0; #5 X1=1; X3=1; #5 X6=1; #5 \$finish; end endmodule </pre> | <h3>Positional Association</h3> <pre> module example (A,B,C,D,E,F,Y); wire t1, t2, t3, Y; nand #1 G1 (t1,A,B); and #2 G2 (t2,C,~B,D); nor #1 G3 (t3,E,F); nand #1 G4 (Y,t1,t2,t3); endmodule </pre> |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|

Hardware Modeling Using Verilog

|                                                                                                                                                                                                                                                                                                                                                                       |                                                                                                                                                                                                   |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre> module testbench; reg X1,X2,X3,X4,X5,X6; wire OUT; example DUT(.OUT(Y),.X1(A),.X2(B),.X3(C), .X4(D),.X5(E),.X6(F));  initial begin \$monitor (\$time," X1=%b, X2=%b, X3=%b, X4=%b, X5=%b, X6=%b, OUT=%b", X1,X2,X3,X4,X5,X6,OUT); #5 X1=1;X2=0; X3=0; X4=1; X5=0; X6=0; #5 X1=0; X3=1; #5 X1=1; X3=0; #5 X1=1; X3=1; #5 X6=1; #5 \$finish; end endmodule </pre> | <h3>Explicit Association</h3> <pre> module example (A,B,C,D,E,F,Y); wire t1, t2, t3, Y; nand #1 G1 (t1,A,B); and #2 G2 (t2,C,~B,D); nor #1 G3 (t3,E,F); nand #1 G4 (Y,t1,t2,t3); endmodule </pre> |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|

Hardware Modeling Using Verilog

### Hardware Modeling Issues

- In terms of the hardware realization, the value computed can be assigned to:
  - A "wire"
  - A "flip-flop" (edge-triggered storage cell)
  - A "latch" (level-triggered storage cell)
- A variable in Verilog can be either "net" or "register".
  - A "net" data type always map to a "wire" during synthesis.
  - A "register" data type maps either to a "wire" or a "storage cell" depending upon the context under which a value is assigned.

Hardware Modeling Using Verilog

```

module reg_maps_to_wire (A, B, C, f1, f2);
input A, B, C;
output f1, f2;
wire A, B, C;
reg f1, f2;
always @(A or B or C)
begin
f1 = ~(A & B);
f2 = f1 ^ C;
end
endmodule

```

The synthesis system will generate a wire for f1.

Hardware Modeling Using Verilog

```

module a_problem_case (A, B, C, f1, f2);
input A, B, C;
output f1, f2;
wire A, B, C;
reg f1, f2;
always @(A or B or C)
begin
f2 = f1 ^ f2;
f1 = ~(A & B);
end
endmodule

```

The synthesis system will generate a wire for f1, and a storage cell for f2.

Hardware Modeling Using Verilog

```

// A latch gets inferred here
module simple_latch (data, load, d_out);
input data, load;
output d_out;
wire t;
always @(load or data)
begin
if (!load)
t = data;
d_out = t;
end
endmodule

```

The "else" part is missing. So a latch will be generated for "t".

Hardware Modeling Using Verilog

## END OF LECTURE 08

## Lecture 09: VERILOG OPERATORS

PROF. INDRANIL SENGUPTA  
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

### Verilog Operators

#### Arithmetic Operators:

- + unary (sign) plus
- unary (sign) minus
- + binary plus (add)
- binary minus (subtract)
- \* multiply
- / divide
- % modulus
- \*\* exponentiation

#### Examples:

```
- (b + c)
(a - b) + (c * d)
(a + b) / (a - b)
a % b
a ** 3
```

#### Logical Operators:

- ! logical negation
- && logical AND
- || logical OR

#### Examples:

```
(done && ack)
(a || b)
!(a && b)
((a > b) || (c == 0))
((a > b) && !(b > c))
```

- The value 0 is treated as logical FALSE while any non-zero value is treated as TRUE.
- Logical operators return either 0 (FALSE) or 1 (TRUE).

#### Relational Operators:

- != not equal
- == equal
- >= greater or equal
- <= less or equal
- > greater
- < less

#### Examples:

```
(a != b)
((a + b) == (c - d))
((a > b) && (c < d))
(count <= 0)
```

Relational operators operate on numbers, and return a Boolean value (true or false).

#### Bitwise Operators:

- ~ bitwise NOT
- & bitwise AND
- | bitwise OR
- ^ bitwise exclusive-OR
- ~^ bitwise exclusive-NOR

#### Examples:

```
wire a, b, c, d, f1, f2, f3, f4;
assign f1 = ~a | b;
assign f2 = (a & b) | (b & c) | (c & a)
assign f3 = a ^ b ^ c;
assign f4 = (a & ~b) | (b & c & ~d);
```

Bitwise operators operate on bits, and return a value that is also a bit.



Reduction operators accepts a single word operand and produce a single bit as output.

- Operates on all the bits within the word.

| Reduction Operators: |                       |
|----------------------|-----------------------|
| &                    | bitwise AND           |
|                      | bitwise OR            |
| ~&                   | bitwise NAND          |
| ~                    | bitwise NOR           |
| ^                    | bitwise exclusive-OR  |
| ~^                   | bitwise exclusive-NOR |

**Examples:**

```
wire [3:0] a, b, c; wire f1, f2, f3;
assign a = 4'b0111;
assign b = 4'b1100;
assign c = 4'b0100;
assign f1 = ^a; // gives a 1
assign f2 = &(a ^ b); // gives a 0
assign f3 = ^a & ~^b; // gives a 1
```

Hardware Modeling Using Verilog

**Shift Operators:**

```
>> shift right
<< shift left
>>> arithmetic shift right
```

**Examples:**

```
wire [15:0] data, target;
assign target = data >> 3;
assign target = data >>> 2;
```

**Conditional Operator:**

```
cond_expr ? true_expr : false_expr;
```

**Examples:**

```
wire a, b, c;
wire [7:0] x, y, z;
assign a = (b > c) ? b : c;
assign z = (x == y) ? x+2 : x-2;
```

Hardware Modeling Using Verilog

**Concatenation Operator:**

```
{..., ..., ...}
```

**Replication Operator:**

```
{n{m}}
```

Joins together n copies of an expression m, where n is a constant.

**Examples:**

```
assign f = {a, b};
assign f = {a, 3'b101, b};
assign f = {x[2], y[0], a};
assign f = {2'b10, 3{2'b01}, x};
```

Hardware Modeling Using Verilog

```
module operator_example (x, y, f1, f2);
input x, y;
output f1, f2;
wire [9:0] x, y; wire [4:0] f1; wire f2;
assign f1 = x[4:0] & y[4:0];
assign f2 = x[2] | ~f1[3];
assign f2 = ~& x;
assign f1 = f2 ? x[9:5] : x[4:0];
endmodule
```

Hardware Modeling Using Verilog

```
// An 8-bit adder description
module parallel_adder (sum, cout, in1, in2, cin);
input [7:0] in1, in2;
input cin;
output [7:0] sum;
output cout;

assign #20 {cout,sum} = in1 + in2 + cin;
endmodule
```

Hardware Modeling Using Verilog

**Operator Precedence**

Operators on same line have the same precedence.

All operators associate left to right in an expression, except ?.

Parentheses can be used to change the precedence.

|                                                                                                                                                  |                                      |
|--------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------|
| <pre> + - ! ~ (unary) ** * / % &lt;&lt; &gt;&gt; &gt;&gt;&gt; &lt; &lt;= &gt; &gt;= == != === !== &amp; ~&amp; ^ ~^   ~  &amp;&amp;    ?: </pre> | <p>↑</p> <p>Precedence increases</p> |
|--------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------|

Hardware Modeling Using Verilog

### Some Points

- The presence of a 'z' or 'x' in a *reg* or *wire* being used in an arithmetic expression results in the whole expression being unknown ('x').
- The logical operators (!, &&, |) all evaluate to a 1-bit result (0, 1 or x).
- The relational operators (>, <, <=, >=, ~=, ==) also evaluate to a 1-bit result (0 or 1).
- Boolean *false* is equivalent to 1'b0.  
Boolean *true* is equivalent to 1'b1.

### END OF LECTURE 09

## Lecture 10: VERILOG MODELING EXAMPLES

PROF. INDRANIL SENGUPTA  
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

### Example 1

- The structural hierarchical description of a 16-to-1 multiplexer.
  - a) Using pure behavioral modeling.
  - b) Structural modeling using 4-to-1 multiplexer specified using behavioral model.
  - c) Make structural modeling of 4-to-1 multiplexer, using behavioral modeling of 2-to-1 multiplexer.
  - d) Make structural gate-level modeling of 2-to-1 multiplexer, to have a complete structural hierarchical description.

#### Version 1: Using pure behavioral modeling

```
module mux16to1 (in, sel, out);
 input [15:0] in;
 input [3:0] sel;
 output out;

 assign out = in[sel];
endmodule
```


Selects one of the input bits depending upon the value of "sel".

```
module muxtest;
 reg [15:0] A; reg [3:0] S; wire F;

 mux16to1 M (.in(A), .sel(S), .out(F));

 initial
 begin
 $dumpfile ("mux16to1.vcd");
 $dumpvars (0,muxtest);
 $monitor ($time, " A=%h, S=%h, F=%b", A,S,F);
 #5 A=16'h3f0a; S=4'h0;
 #5 S=4'h1;
 #5 S=4'h6;
 #5 S=4'hc;
 #5 $finish;
 end
endmodule
```

 
```
0 A=xxxx, S=x, F=x
5 A=3f0a, S=0, F=0
10 A=3f0a, S=1, F=1
15 A=3f0a, S=6, F=0
20 A=3f0a, S=c, F=1
```


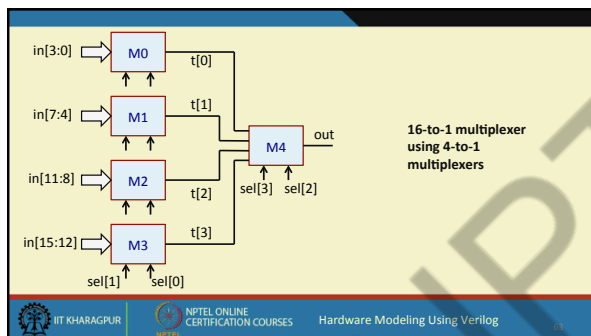
### Version 2: Behavioral modeling of 4-to-1 MUX Structural modeling of 16-to-1 MUX

```
module mux4to1 (in, sel, out);
 input [3:0] in;
 input [1:0] sel;
 output out;
 assign out = in[sel];
endmodule
```


```
module mux16to1 (in, sel, out);
 input [15:0] in;
 input [3:0] sel;
 output out;
 wire [3:0] t;
 mux4to1 M0 (in[3:0], sel[1:0], t[0]);
 mux4to1 M1 (in[7:4], sel[1:0], t[1]);
 mux4to1 M2 (in[11:8], sel[1:0], t[2]);
 mux4to1 M3 (in[15:12], sel[1:0], t[3]);
 mux4to1 M4 (t, sel[2:3], out);
endmodule
```


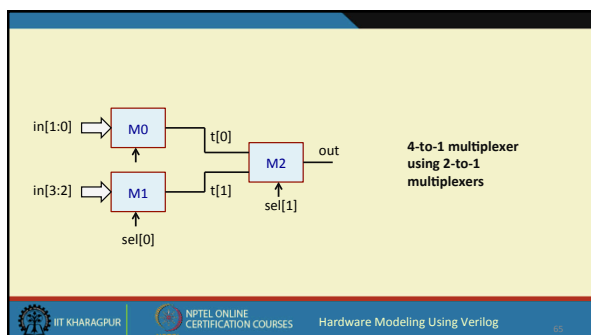
### Version 3: Behavioral modeling of 2-to-1 MUX Structural modeling of 4-to-1 MUX

```
module mux2to1 (in, sel, out);
 input [1:0] in;
 input [1:0] sel;
 output out;
 assign out = in[sel];
endmodule
```

```
module mux4to1 (in, sel, out);
 input [3:0] in;
 input [1:0] sel;
 output out;
 wire [1:0] t;
 mux2to1 M0 (in[1:0], sel[0], t[0]);
 mux2to1 M1 (in[3:2], sel[0], t[1]);
 mux2to1 M2 (t, sel[1], out);
endmodule
```



### Version 4: Structural modeling of 2-to-1 MUX

```
module mux2to1 (in, sel, out);
 input [1:0] in;
 input sel;
 output out;
 wire t1, t2, t3;
 NOT G1 (t1, sel);
 AND G2 (t2, in[0], t1);
 AND G3 (t3, in[1], sel);
 OR G4 (out, t2, t3);
endmodule
```

#### Point to note:

- Same test bench can be used for all the versions.
- The versions illustrate hierarchical refinement of design.

## END OF LECTURE 10

## Lecture 11: VERILOG MODELING EXAMPLES (contd.)

PROF. INDRANIL SENGUPTA  
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

### Example 2

#### Version 1: Behavioral description of a 16-bit adder.

- Generation of status flags:
  - Sign : whether the sum is negative or positive
  - Zero : whether the sum is zero
  - Carry : whether there is a carry out of the last stage
  - Parity : whether the number of 1's in the sum is even or odd
  - Overflow : whether the sum cannot fit in 16 bits

```
module ALU (X, Y, Z, Sign, Zero, Carry, Parity, Overflow);
 input [15:0] X, Y;
 output [15:0] Z;
 output Sign, Zero, Carry, Parity, Overflow;

 assign {Carry, Z} = X + Y; // 16-bit addition
 assign Sign = Z[15];
 assign Zero = ~Z;
 assign Parity = ~^Z;
 assign Overflow = (X[15] & Y[15] & ~Z[15]) |
 (~X[15] & ~Y[15] & Z[15]);


endmodule
```

```
module alutest;
 reg [15:0] X, Y;
 wire [15:0] Z; wire S, ZR, CY, P, V;
 ALU DUT (X, Y, Z, S, ZR, CY, P, V);

 initial
 begin
 $dumpfile ("alu.vcd"); $dumpvars (0, alutest);
 $monitor ($time, " X=%h, Y=%h, Z=%h, S=%b, ZR=%b, CY=%b, P=%b, V=%b",
 X, Y, Z, S, ZR, CY, P, V);
 #5 X = 16'h8fff; Y = 16'h8000;
 #5 X = 16'hffff; Y = 16'h0002;
 #5 X = 16'hAAAA; Y = 16'h5555;
 #5 $finish;
 end
endmodule
```
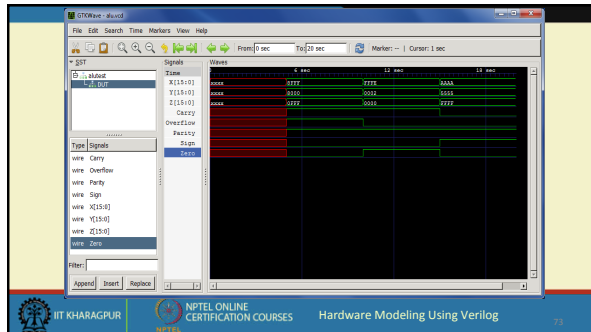
### Simulation Output

```
0 X=xxxx, Y=xxxx, Z=xxxx, S=x, ZR=x, CY=x, P=x, V=x
5 X=8fff, Y=8000, Z=0fff, S=0, ZR=0, CY=1, P=1, V=1
10 X=ffff, Y=0002, Z=0000, S=0, ZR=1, CY=1, P=1, V=0
15 X=aaaa, Y=5555, Z=ffff, S=1, ZR=0, CY=0, P=1, V=0
```



### Version 2: Structural description of 16-bit adder using 4-bit adder blocks (with ripple carry between blocks).

```
module ALU (X, Y, Z, Sign, Zero, Carry, Parity, Overflow);
 input [15:0] X, Y;
 output [15:0] Z;
 output Sign, Zero, Carry, Parity, Overflow;
 wire c[3:1];

 assign Sign = Z[15];
 assign Zero = ~|Z;
 assign Parity = ~^Z;
 assign Overflow = (X[15] & Y[15] & ~Z[15]) |
 (~X[15] & ~Y[15] & Z[15]);
 .. Contd.
endmodule
```

```
adder4 A0 (Z[3:0], c[1], X[3:0], Y[3:0], 1'b0);
adder4 A1 (Z[7:4], c[2], X[7:4], Y[7:4], c[1]);
adder4 A2 (Z[11:8], c[3], X[11:8], Y[11:8], c[2]);
adder4 A3 (Z[15:12], Carry, X[15:12], Y[15:12], c[3]);
endmodule
```

#### Behavioral description of a 4-bit adder

```
module adder4 (S, cout, A, B, cin);
 input [3:0] A, B; input cin;
 output [3:0] S; output cout;

 assign {cout,S} = A + B + cin;
endmodule
```


### Version 3: Structural Modeling of Ripple Carry Adder

```
module adder4 (S, cout, A, B, cin);
 input [3:0] A, B; input cin;
 output [3:0] S; output cout;
 wire c1,c2,c3;

 fulladder FA0 (S[0],c1,A[0],B[0],cin);
 fulladder FA1 (S[1],c2,A[1],B[1],c1);
 fulladder FA2 (S[2],c3,A[2],B[2],c2);
 fulladder FA3 (S[3],cout,A[3],B[3],c3);
endmodule
```

```
module fulladder (s, cout, a, b, c);
 input a, b, c;
 output s, cout;
 wire s1,c1,c2;

  xor G1 (s1,a,b), G2 (s,s1,c),
 G3 (cout,c2,c1);
 and G4 (c1,a,b), G5 (c2,s1,c);
endmodule
```



### Version 4: Structural Modeling of Carry Lookahead Adder

```
module adder4 (S, cout, A, B, cin);
 input [3:0] A, B; input cin;
 output [3:0] S; output cout;
 wire p0, g0, p1, g1, p2, g2, p3, g3;
 wire c1, c2, c3;

 assign p0 = A[0] ^ B[0], p1 = A[1] ^ B[1],
 p2 = A[2] ^ B[2], p3 = A[3] ^ B[3];

 assign g0 = A[0] & B[0], g1 = A[1] & B[1],
 g2 = A[2] & B[2], g3 = A[3] & B[3];
 .. Contd..
endmodule
```

```

assign c1 = g0 | (p0 & cin),
 c2 = g1 | (p1 & g0) | (p1 & p0 & cin),
 c3 = g2 | (p2 & g1) | (p2 & p1 & g0) | (p2 & p1 & p0 & cin),
 cout = g3 | (p3 & g2) | (p3 & p2 & g1) | (p3 & p2 & p1 & g0) |
 (p3 & p2 & p1 & p0 & cin);

assign S[0] = p0 ^ cin,
 S[1] = p1 ^ c1,
 S[2] = p2 ^ c2,
 S[3] = p3 ^ c3;

endmodule

```

Hardware Modeling Using Verilog

### How does a Carry Look-ahead Adder work?

- The propagation delay of an n-bit ripple carry order is proportional to n.
  - Due to the rippling effect of carry sequentially from one stage to the next.
- One possible way to speedup the addition.
  - Generate the carry signals for the various stages in parallel.
  - Time complexity reduces from  $O(n)$  to  $O(1)$ .
  - Hardware complexity increases rapidly with n.

Hardware Modeling Using Verilog

- Consider the i-th stage in the addition process.
- We define the *carry generate* and *carry propagate* functions as:
 
$$g_i = A_i \cdot B_i$$

$$p_i = A_i \oplus B_i$$
- $g_i = 1$  represents the condition when a carry is generated in stage-i independent of the other stages.
- $p_i = 1$  represents the condition when an input carry  $C_i$  will be propagated to the output carry  $c_{i+1}$ .

Hardware Modeling Using Verilog

### Unrolling the Recurrence

$$\begin{aligned}
 C_{i+1} &= g_i + p_i \cdot C_i = g_i + p_i (g_{i-1} + p_{i-1} C_{i-1}) = g_i + p_i g_{i-1} + p_i p_{i-1} C_{i-1} \\
 &= g_i + p_i g_{i-1} + p_i p_{i-1} (g_{i-2} + p_{i-2} C_{i-2}) \\
 &= g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + p_i p_{i-1} p_{i-2} C_{i-2} = \dots
 \end{aligned}$$

$$C_{i+1} = g_i + \sum_{k=0}^{i-1} g_k \prod_{j=k+1}^i p_j + c_0 \prod_{j=0}^i p_j$$

Hardware Modeling Using Verilog

### Generation of the Carry and Sum bits

$$\begin{aligned}
 C_4 &= g_3 + g_2 p_3 + g_1 p_2 p_3 + g_0 p_1 p_2 p_3 + c_0 p_0 p_1 p_2 p_3 \\
 C_3 &= g_2 + g_1 p_2 + g_0 p_1 p_2 + c_0 p_0 p_1 p_2 \\
 C_2 &= g_1 + g_0 p_1 + c_0 p_0 p_1 \\
 C_1 &= g_0 + c_0 p_0
 \end{aligned}$$

4 AND2 gates  
3 AND3 gates  
2 AND4 gates  
1 AND5 gate  
1 OR2, 1 OR3, 1 OR4 and 1 OR5 gate

$$\begin{aligned}
 S_0 &= A_0 \oplus B_0 \oplus C_0 = p_0 \oplus C_0 \\
 S_1 &= p_1 \oplus C_1 \\
 S_2 &= p_2 \oplus C_2 \\
 S_3 &= p_3 \oplus C_3
 \end{aligned}$$

4 XOR2 gates

Hardware Modeling Using Verilog

Hardware Modeling Using Verilog

