

# EC-204

## <LAB - 7>

### NITK SURATHKAL



### INBASEKARAN.P

## 201EC226

### Prof: Sumam S

## 1. Decade Counter

### Solution:


#### a) Code

```


question1 > question1.v
1  module decadeUpDown (count_up, load, reset, counter_on, data_in,clk, count, TC);
2      input count_up, load, reset, counter_on;
3      input [3:0]data_in; input clk;
4      output reg [3:0]count; output reg TC;
5      always @(posedge clk, negedge reset) begin
6          if(reset == 1)
7              count <= 0;
8              // If the load = 1, the data data_in is loaded into the counter.
9          else if(load == 1)
10             count <= data_in;
11         else if(counter_on == 1)
12             begin
13                 if(count_up == 1)
14                     count <= count + 1;
15                 else
16                     count <= count - 1;
17             end
18             // If the counter_on=counter_up=1, the counter is incremented, the Terminal carry
19             // output TC=1 when the counter is in state 9.
20
21             if(count_up == 1 && count == 9)
22                 begin
23                     TC <= 1;
24                     count <= 0;
25                 end
26             // If the counter_on=1 and counter_up=0, the counter is decremented, the Terminal
27             // carry output TC=1 when the counter is in state 0.
28             else if(count_up == 0 && count == 0)
29                 begin
30                     TC <= 1;
31                     count <= 9;
32                 end
33             else
34                 TC <= 0;
35         end
36     endmodule

```

## Simulation waveform UP Count

 

## Simulation waveform DOWN Count

 


## 2. Decimal up down counter

### Solution:


### Verilog code

```
question2 > question2.fv
1 module twoDigitDecadeCounter(input counter_up,
2   input load, input reset, input counter_on, input clk, input [7:0] data_in,
3   output [7:0] count, output TC);
4   wire n1;
5   decadeCounter cunit(counter_up, load, reset, counter_on, clk, data_in[3:0], count[3:0], n1);
6   decadeCounter cdigit(counter_up, load, reset, counter_on, n1, data_in[7:4], count[7:4], TC);
7 endmodule
```

## Simulation UP count

 

## Simulation DOWN count

 


## 3. N bit program counter

### Solution:

### Verilog code

```
question3 > question3.v
1  module up_counter_nbit(R, Resetn, Clk, PCinc, PCload,
2      parameter n = 4;
3      input [n-1:0] R;
4      input Resetn, Clk, PCload, PCinc;
5      output reg [n-1:0] Q;
6      always@(negedge Resetn, posedge Clk)
7          if (!Resetn)
8              Q <= 0;
9          else if (PCload)
10             Q <= R;
11             else if (PCinc)
12                 Q <= Q + 1;
13 endmodule
```

## Simulation waveform

 

## 4. Shift Register 74194

**Solution:**

Verilog code


```
question4 > question4.v
1  module universalShiftReg(din,S,clk,Q, reset, lsi, rsi,P);
2      input [3:0]din;
3      input [3:0]P;
4      input [1:0]S;
5      input reset, clk, lsi, rsi;
6      output reg [3:0]Q;
7      assign Q = din;
8      wire [3:0]din;
9      always@(posedge clk, negedge reset)
10         if (!reset)
11             Q <= 4'b0000;
12         else
13             begin
14                 Q <= din;
15                 case (S)
16                     // no change
17                     2'b00:
18                         begin
19                             Q[3] <= Q[3];
20                             Q[2] <= Q[2];
21                             Q[1] <= Q[1];
22                             Q[0] <= Q[0];
23                         end
24                     // shift right
25                     2'b01:
26                         begin
27                             Q[3] <= rsi;
28                             Q[2] <= Q[3];
29                             Q[1] <= Q[2];
30                             Q[0] <= Q[1];
31                         end
32                     // shift left
33                     2'b10:
34                         begin
35                             Q[0] <= lsi;
36                             Q[1] <= Q[0];
37                             Q[2] <= Q[1];
```

```

25         2'b01:
26             begin
27                 Q[3] <= rsi;
28                 Q[2] <= Q[3];
29                 Q[1] <= Q[2];
30                 Q[0] <= Q[1];
31             end
32             // shift left
33         2'b10:
34             begin
35                 Q[0] <= lsi;
36                 Q[1] <= Q[0];
37                 Q[2] <= Q[1];
38                 Q[3] <= Q[2];
39             end
40             // load
41         2'b11:
42             begin
43                 Q[3] <= P[3];
44                 Q[2] <= P[2];
45                 Q[1] <= P[1];
46                 Q[0] <= P[0];
47             end
48         endcase
49     end
50 endmodule

```

### Simulation waveform

 


## 5. Self-correction ring counter

### Solution:

### Verilog code

```
question5 > question5.v
1  module ring_counter(
2      Clock,
3      Reset,
4      Count
5  );
6      input Clock;
7      input Reset;
8      output [3:0] Count;
9      reg [3:0] Count_temp;
10     always @(posedge(Clock),Reset)
11     begin
12         if(Reset == 1'b1 || Count == 4'b0000 || Count == 4'b1000)
13         begin
14             Count_temp = 4'b0001;
15         end
16         else if(Clock == 1'b1)
17         begin
18             Count_temp = {Count_temp[2:0],Count_temp[3]};
19         end
20     end
21     assign Count = Count_temp;
22 endmodule
23
```

### Simulation waveform

 

## 6. Pseudo random sequence generator

### Solution:

### Verilog code

```
question6 > V question6.v
1  module pseudoRandomSeqGenerator( resetn, clk, Q);
2      parameter n =8;
3      input resetn, clk;
4      output reg [n-1:0] Q;
5      always @(negedge resetn, posedge clk)
6      begin
7          if(!resetn) Q<={1'b1, {n-2{1'b0}}};
8          else begin
9              Q <= Q >> 1;
10             Q[n-1] <= Q[7] ^ Q[3] ^ Q[2] ^Q[1];
11         end
12     end
13 endmodule
14
```

### Simulation waveform

