

EC-204

<LAB- 4>

NITK SURATHKAL



INBASEKARAN.P

201EC226

Prof: Sumam S

1. 2 to 4 decoder using (a) concurrent signal assignment statements (b) case statement

Solution:


a) Concurrent Signal assignments

```

dec2to4.v
1  module dec2to4(a, En, Y);
2      input [1:0] a;
3      input En;
4      output reg [3:0] Y;
5      /*
6       // Can be done using multiple assign statements
7       assign Y[0] = (En & ~a[1] & ~a[0]);
8       assign Y[1] = (En & ~a[1] & a[0]);
9       assign Y[2] = (En & a[1] & ~a[0]);
10      assign Y[3] = (En & a[1] & a[0]);
11      */
12      // or a short version with one assign statement
13      // When enable is one 1 is right shifted by a bits
14      assign Y = En ? (1<<a) : (4'b0000);
15  endmodule

```


Simulation waveform

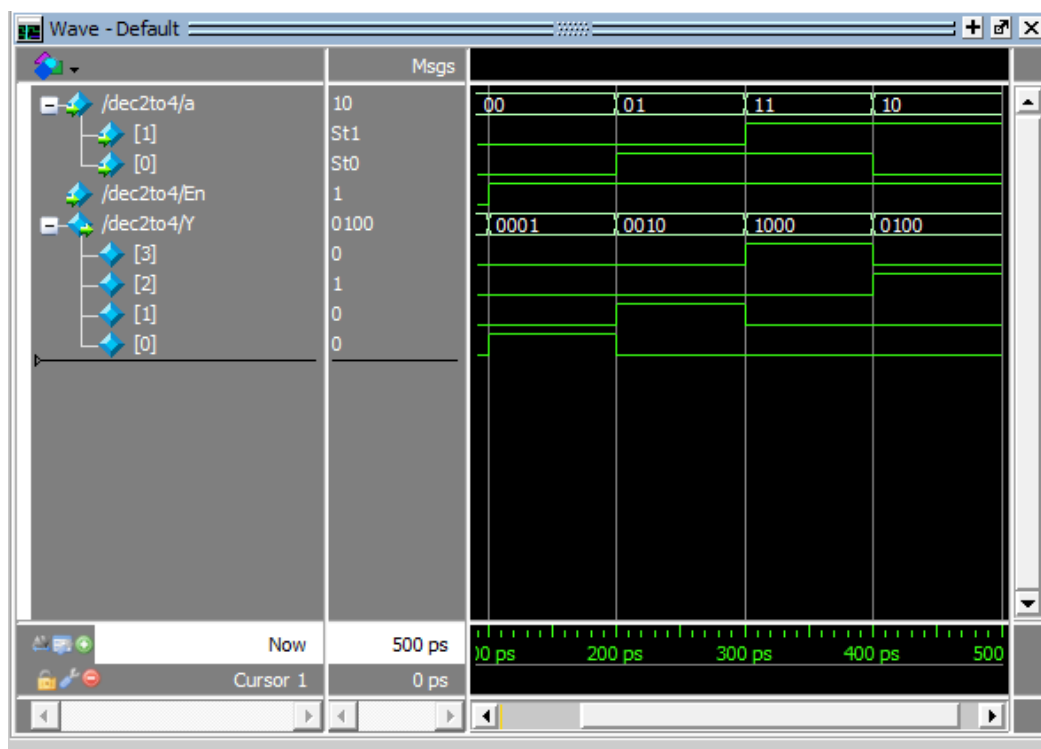

b) Case statements

```
dec2to4_case.v
1  module dec2to4_case (W, En, Y);
2  // input lines 2 bit
3  |   input [1:0] W;
4  // enable input
5  |   input En;
6  // output line 4 bit
7  |   output reg [0:3] Y;
8  |   always @(W, En)
9  |       begin
10 |           // if enable is 0 then output is always 0
11 |           if (En == 0)
12 |               Y = 4'b0000;
13 |           else
14 |               case (W)
15 |                   // output mapped according to the truth table
16 |                   0: Y = 4'b1000;
17 |                   1: Y = 4'b0100;
18 |                   2: Y = 4'b0010;
19 |                   3: Y = 4'b0001;
20 |               endcase
21 |           end
22 |   endmodule
23
```

Simulation waveform

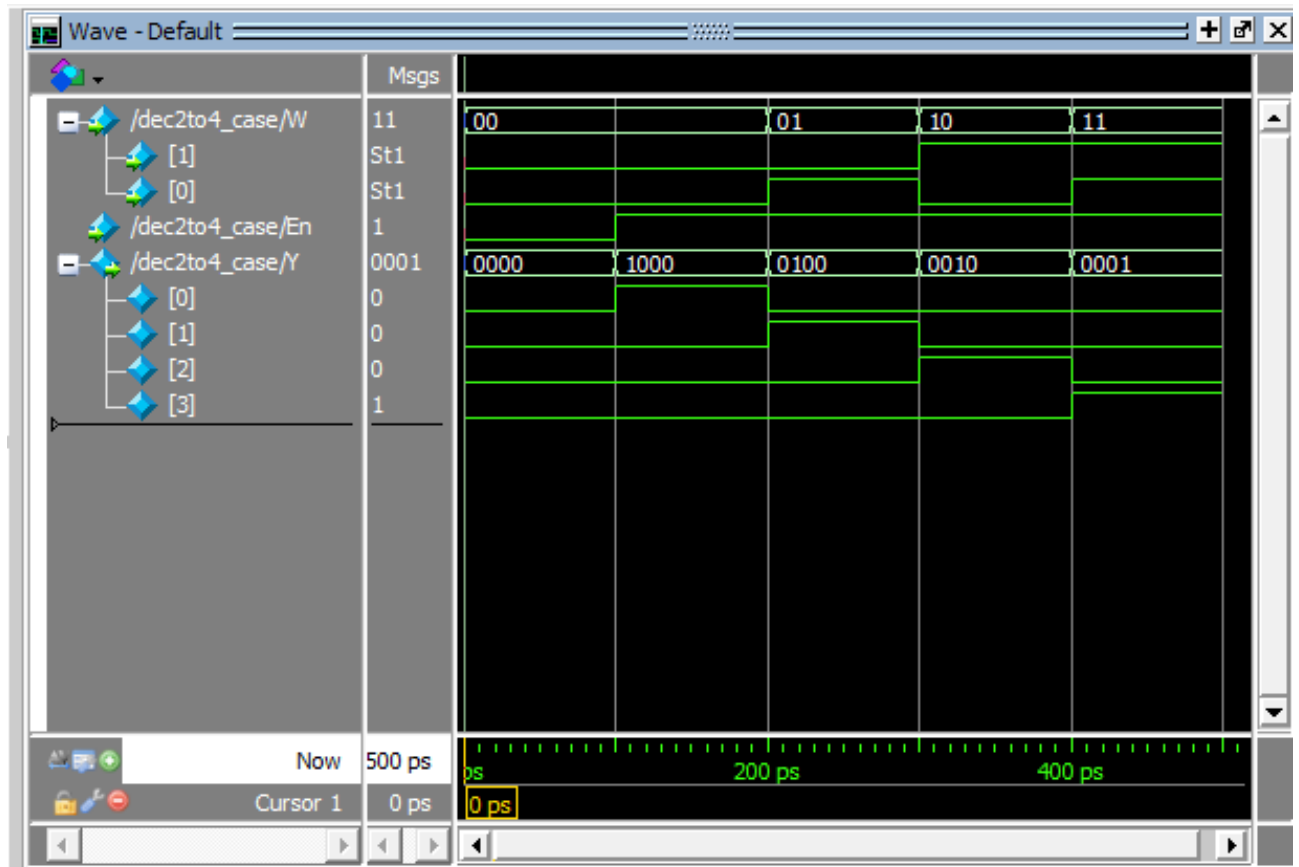


2. 16:1 Mux

Solution:

Verilog code

```
question2 > mux16_1.v
1  module mux16_1(I,S,Y);
2  // input I 16 bit
3  |   input [15:0] I;
4  // selector 4 bit
5  |   input [3:0] S;
6  // output Y
7  |   output reg Y;
8  // Bit Select operation
9  |   assign Y = I[S];
10 |   endmodule
```

Simulation

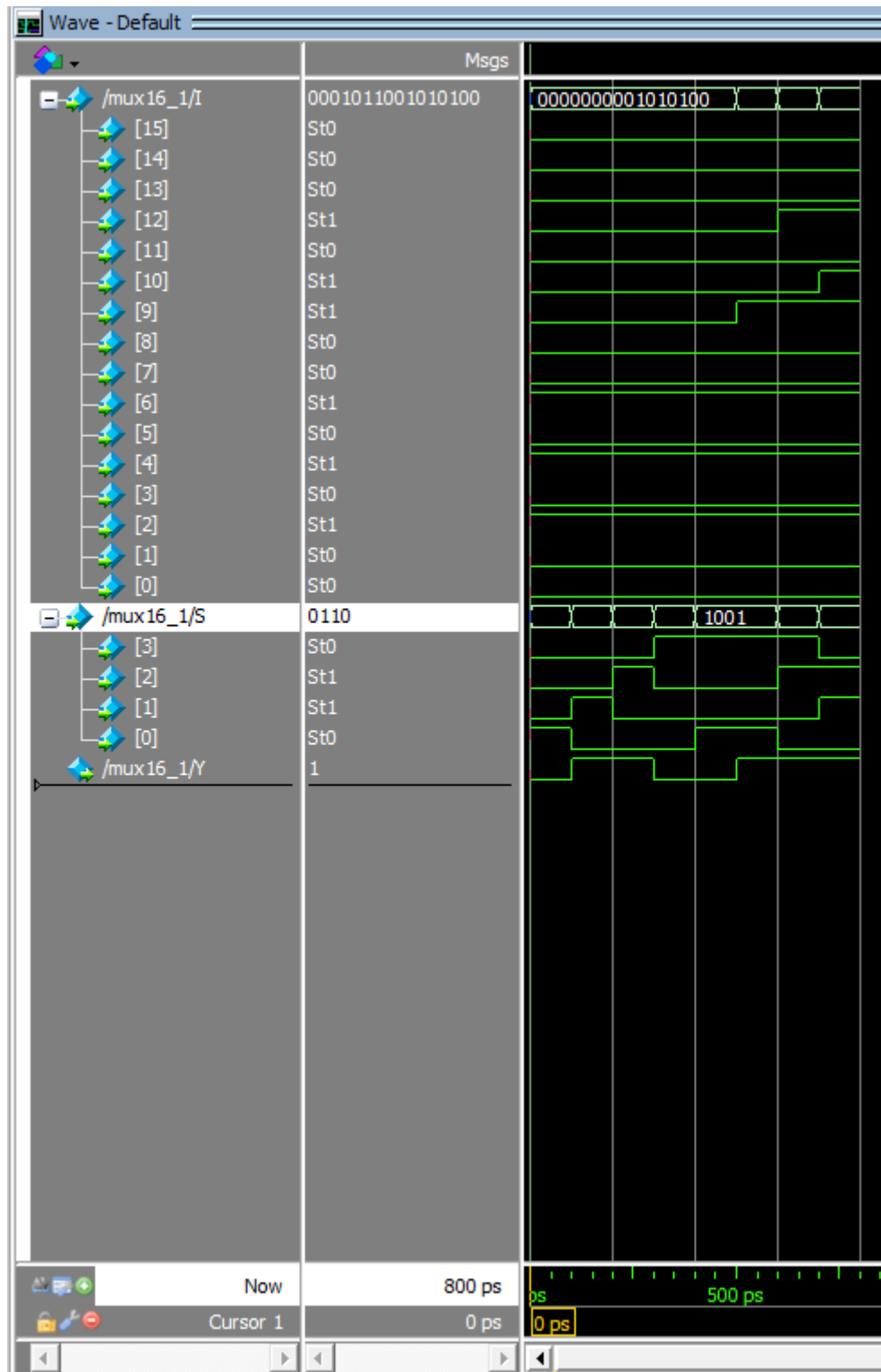

3. Functionality of 74x148 priority encoder

Solution:

Verilog code

question3 >  priority.v

```

1  module priority(E, I, A, GS, EO);
2      input E; input [7:0]I;
3      output reg [2:0]A;
4      output reg GS;
5      output reg EO;
6      always @(E, I) begin
7          // active low enable
8          if(E == 1)
9              begin
10                 GS = 1;
11                 EO = 1;
12                 A = 3'd7;
13             end
14         else
15             begin
16                 // cases for all the inputs acc to the truth table
17                 casex (I)
18                     8'bxxxxxx0: begin
19                         A = 0;
20                         GS = 0;
21                         EO = 1;
22                     end
23                     8'bxxxxxx01: begin
24                         A = 3'd1;
25                         GS = 0;
26                         EO = 1;
27                     end
28                     8'bxxxxxx011: begin
29                         A = 3'd2;
30                         GS = 0;
31                         EO = 1;


```

```


29         A = 3'd2;
30         GS = 0;
31         EO = 1;
32     end
33     8'bxxxx0111: begin
34         A = 3'd3;
35         GS = 0;
36         EO = 1;
37     end
38     8'bxxx01111: begin
39         A = 3'd4;
40         GS = 0;
41         EO = 1;
42     end
43     8'bx011111: begin
44         A = 3'd5;
45         GS = 0;
46         EO = 1;
47     end
48     8'bx0111111: begin
49         A = 3'd6;
50         GS = 0;
51         EO = 1;
52     end
53     8'b01111111: begin
54         A = 3'd7;
55         GS = 0;
56         EO = 1;
57     end
58     8'b11111111: begin
59         A = 3'd7;
60         GS = 1;
61         EO = 0;
62     end
63 endcase
64 end
65 end
66 endmodule
67
68

```

Simulation waveform

 

4. ALU design

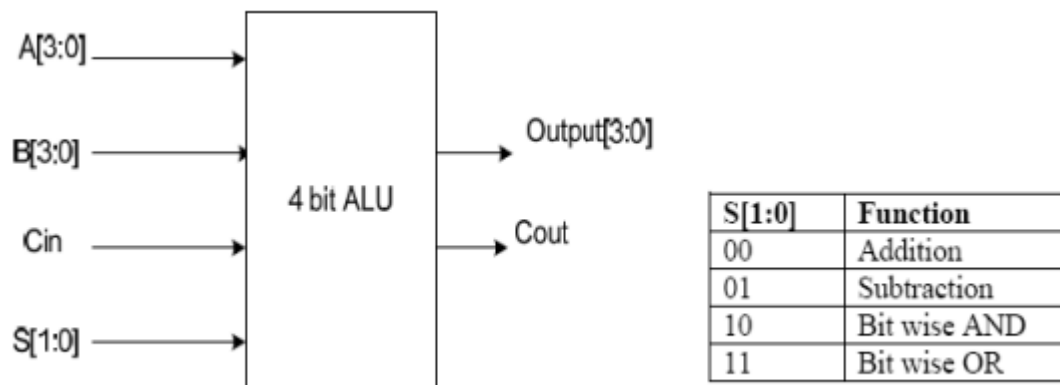


Solution:


Verilog code

```
question4 > V alu.v
1  module alu ( A, B, Cin, S, O, Cout);
2      input [3:0] A,B;
3      input Cin;
4      input [1:0]S;
5      reg [4:0] Y;
6      output reg [3:0] O;
7      output reg Cout;
8      always @(A,B,Cin,S) begin
9          // case for the given selector variable
10         case(S)
11             // addn
12             0 : Y = A + B + Cin;
13             // sub
14             1 : Y = A - B - Cin;
15             // bitwise and
16             2 : Y = A & B;
17             // bitwise or
18             3 : Y = A | B;
19         endcase
20         // assigning output to Cout and O
21         {Cout, O} = Y;
22     end
23 endmodule
```


Simulation waveform for S = 00

 


Simulation waveform for S = 01

 

Simulation waveform for S = 10

 

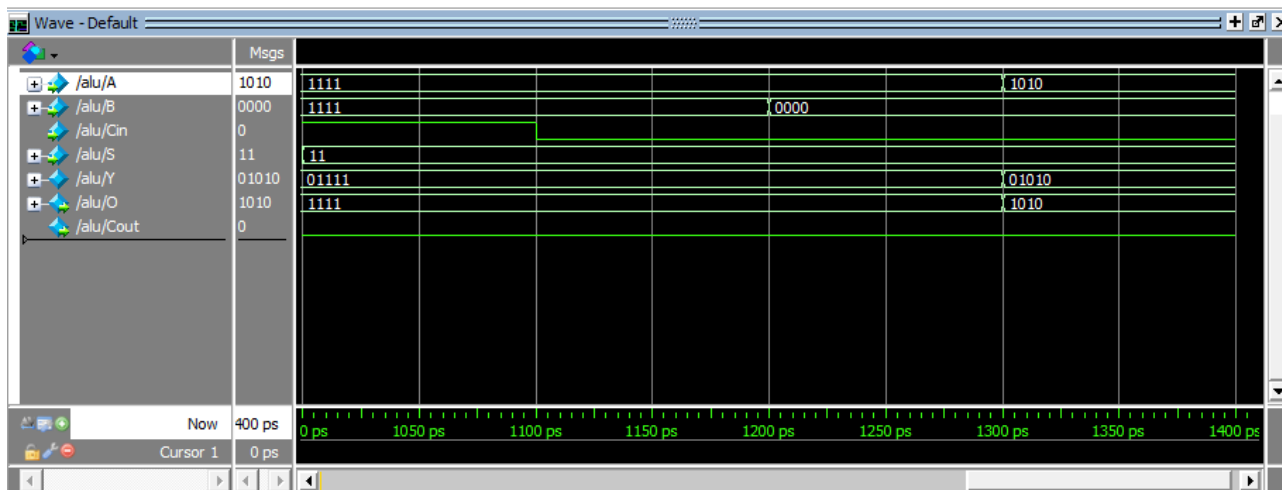Simulation waveform for $S = 11$ 


5. Count number of 1s in a 32-bit number.

Solution:

Verilog code

```
question5 > V ones_count.v
1  module ones_count(A, ones);
2      input [31:0] A;
3      output reg [5:0] ones;
4      integer i;
5      always@(A)
6          begin
7              ones = 0; //initialize count variable.
8              for(i=0;i<32;i=i+1) //for all the bits.
9                  ones = ones + A[i]; //Add the bit to the count.
10         end
11     endmodule
12
```

Simulation waveform

 

6. Implement the following function


$F(v,w,x,y,z) = \Sigma (0, 2, 3, 4, 8, 21, 22, 29, 31)$

Solution:

Verilog code

```
question6 > V fun.v
1  module fun(A,B,C,D,E,F);
2      input A,B,C,D,E;
3      output reg F;
4      always @(A,B,C,D,E) begin
5          // setting the value of F to 1 for the min terms
6          case ({A,B,C,D,E})
7              0 : F = 1'b1;
8              2 : F = 1'b1;
9              3 : F = 1'b1;
10             4 : F = 1'b1;
11             8 : F = 1'b1;
12             21 : F = 1'b1;
13             22 : F = 1'b1;
14             29 : F = 1'b1;
15             31 : F = 1'b1;
16             // setting the value as 0 for others
17             default: F = 0;
18         endcase
19     end
20 endmodule
```

Simulation waveform

 


7. 16-bit magnitude comparator.

Solution:

Verilog code

```
question7 > magComp.v
1  module magComp ( In1, In2, Gt, Lt, Eq );
2      input [15:0] In1, In2; //The two 16-bit Inputs In1 and In2
3      output reg  Gt, Lt, Eq; //The Outputs of comparison
4      always @ (In1 or In2) //Check the state of the input lines
5      begin
6          Gt <= ( In1 > In2 )? 1'b1 : 1'b0;
7          Lt <= ( In1 < In2 )? 1'b1 : 1'b0;
8          Eq <= ( In1 == In2)? 1'b1 : 1'b0;
9      end
10 endmodule
```


Simulation waveform

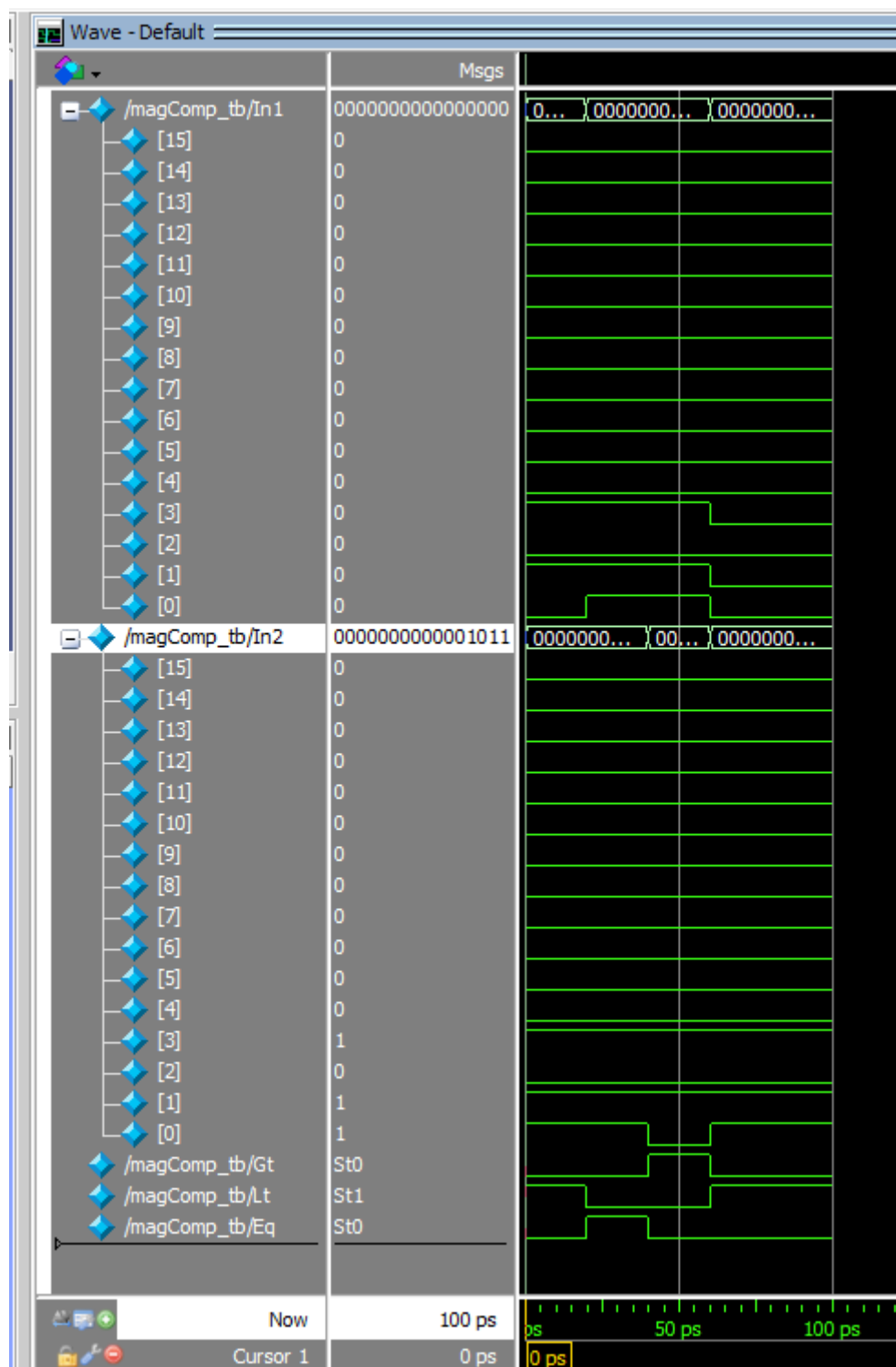

8. Count the number of leading 0's in an 8-bit number.

Solution:

Verilog code

```
question8 >  zero_count_beg.v
1  module zero_count_beg(A, zeros);
2      input [0:7] A;
3      output reg [3:0] zeros;
4      integer i;
5      always@(A)
6          begin
7              zeros = 0; //initialize count variable.
8              for(i=0; i<8 && A[i] == 1'b0; i=i+1) //for all the bits.
9                  begin
10                     zeros = zeros + 1;
11                 end
12          end
13 endmodule
14
```

Simulation waveform

