

EC-204

<LAB - 3>

NITK SURATHKAL



INBASEKARAN.P

201EC226

Prof: Sumam S

1. Design a circuit to convert 4 bits Binary to Gray and 4 bits Gray to Binary Code using XOR gates

Solution:

Binary to Gray

TRUTH TABLE

B3	B2	B1	B0	G3	G2	G1	G0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

KMAP

Output:

Format:

B1, B0

		00	01	11	10
B3, B2	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	1	1	1	1

B3

Output:

Format:

B1, B0

		00	01	11	10
B3, B2	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	1	1

$\overline{B3} \overline{B2} + B3 \overline{B2}$

Output: G1

Format: Sum of products

B1, B0

	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

$\overline{B2} B1 + B2 \overline{B1}$

Output: G0

Format: Sum of products


B1, B0

	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1


$\overline{B1} B0 + B1 \overline{B0}$

EXPLAIN

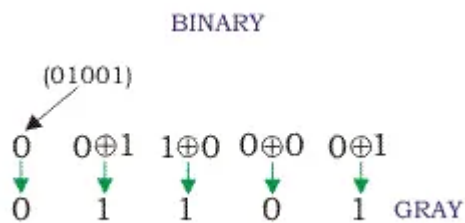
The Binary to Gray code the MSB remains same and the other bits can be calculated by XOR with the adjacent bits.



CIRCUIT

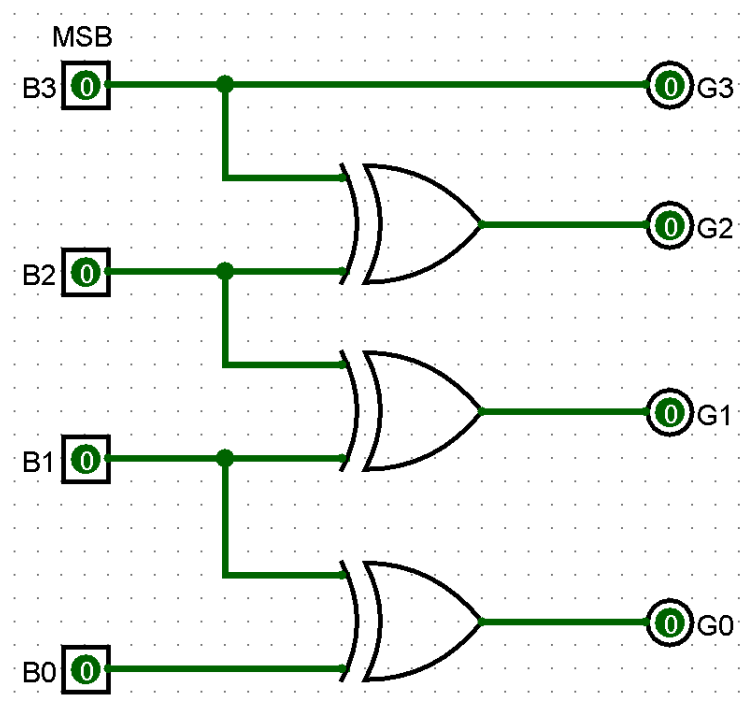





RESULT OBTAINED

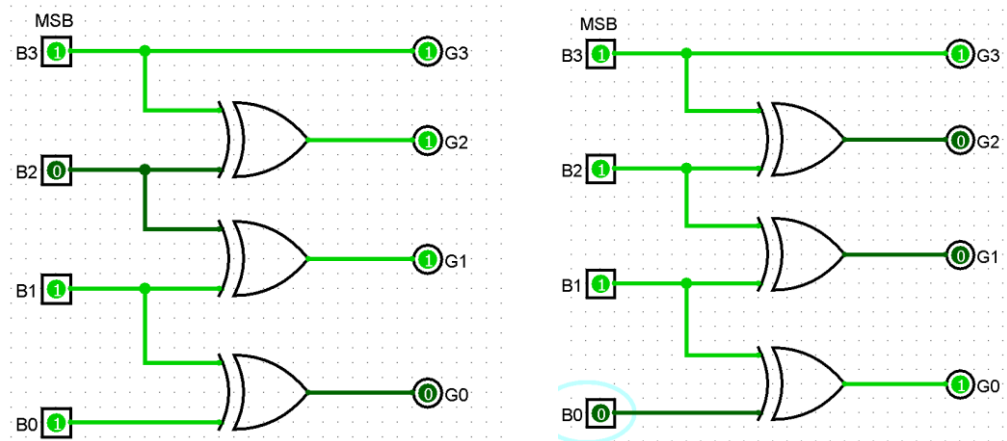


Gray to Binary Code




TURTH TABLE

G3	G2	G1	G0	B3	B2	B1	B0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	1	0

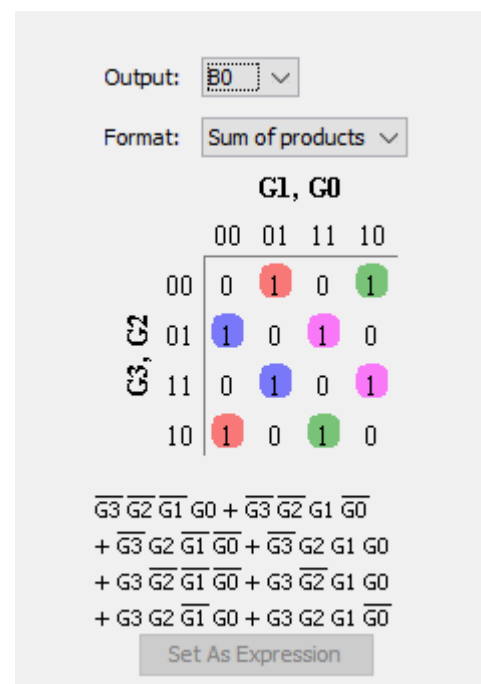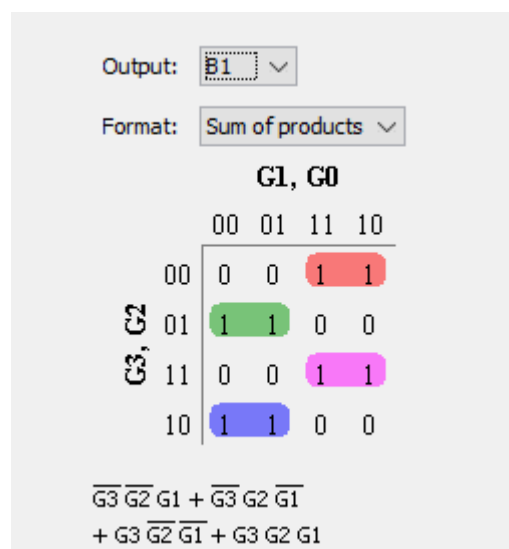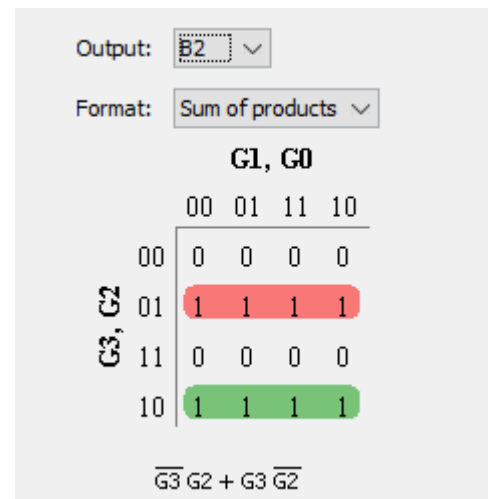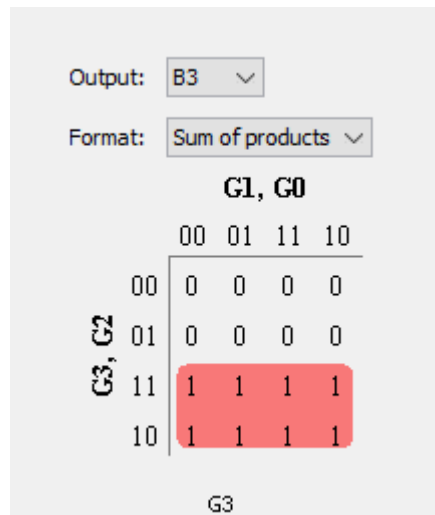KMAPEXPLAIN

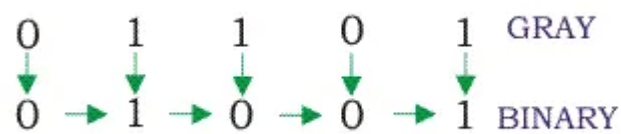The Gray code to Binary the MSB remains same and the other bits can be calculated by XOR as follows



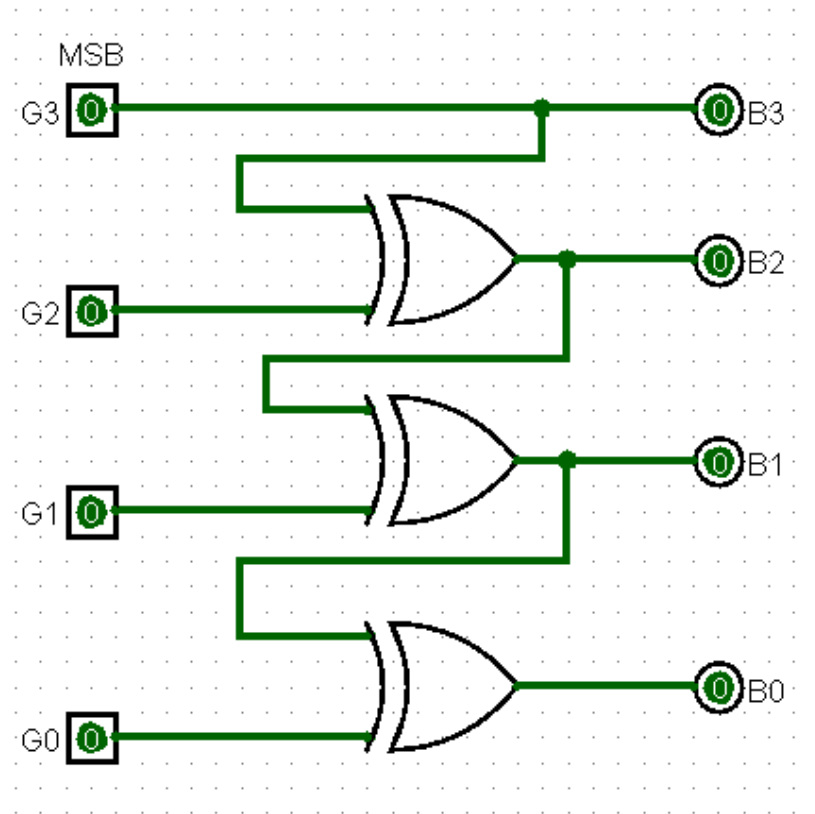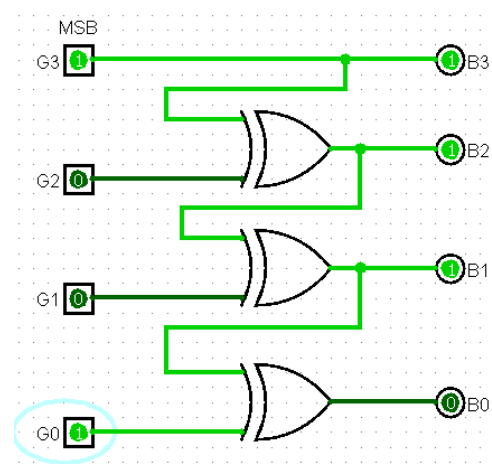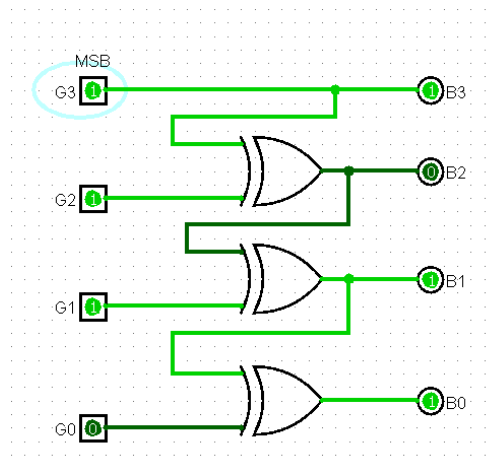CIRCUITRESULT OBTAINED

2. Design an Excess-3 to BCD code converter and implement using 8:1 multiplexer. Use the multiplexer available in Plexers library in logisim.

Solution:

TURTH TABLE

X3	X2	X1	X0	Y3	Y2	Y1	Y0
0	0	0	0	x	x	x	x
0	0	0	1	x	x	x	x
0	0	1	0	x	x	x	x
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	1	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	0	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

EXPLAIN

Excess-3 binary code is an unweighted self-complementary BCD code.

Self-Complementary property means that the 1's complement of an excess-3 number is the excess-3 code of the 9's complement of the corresponding decimal number. This property is useful since a decimal number can be nines' complemented (for subtraction) as easily as a binary number can be ones' complemented; just by inverting all bits.

For example, the excess-3 code for 3(0011) is 0110 and to find the excess-3 code of the complement of 3, we just need to find the 1's complement of 0110 -> 1001, which is also the excess-3 code for the 9's complement of 3 -> $(9-3) = 6$.

KMAP

Output: Y3

Format: Sum of products

X1, X0

X3, X2

00	x	x	0	x
01	0	0	0	0
11	1	x	x	x
10	0	0	1	0

X3 X1 X0 + X3 X2

Set As Expression

Output: Y2

Format: Sum of products

X1, X0

X3, X2

00	x	x	0	x
01	0	0	1	0
11	0	x	x	x
10	1	1	0	1

$\overline{X2} \overline{X1} + \overline{X2} \overline{X0} + X2 X1 X0$

Set As Expression

Output: Y1

Format: Sum of products

X1, X0

X3, X2

00	x	x	0	x
01	0	1	0	1
11	0	x	x	x
10	1	1	0	0

$\overline{X2} \overline{X1} + \overline{X1} X0 + \overline{X3} X1 \overline{X0}$

Set As Expression

Output: Y0

Format: Sum of products


X1, X0



X3, X2

00	x	x	0	x
01	1	0	0	1
11	1	x	x	x
10	1	0	0	1

$\overline{X0}$

CIRCUIT

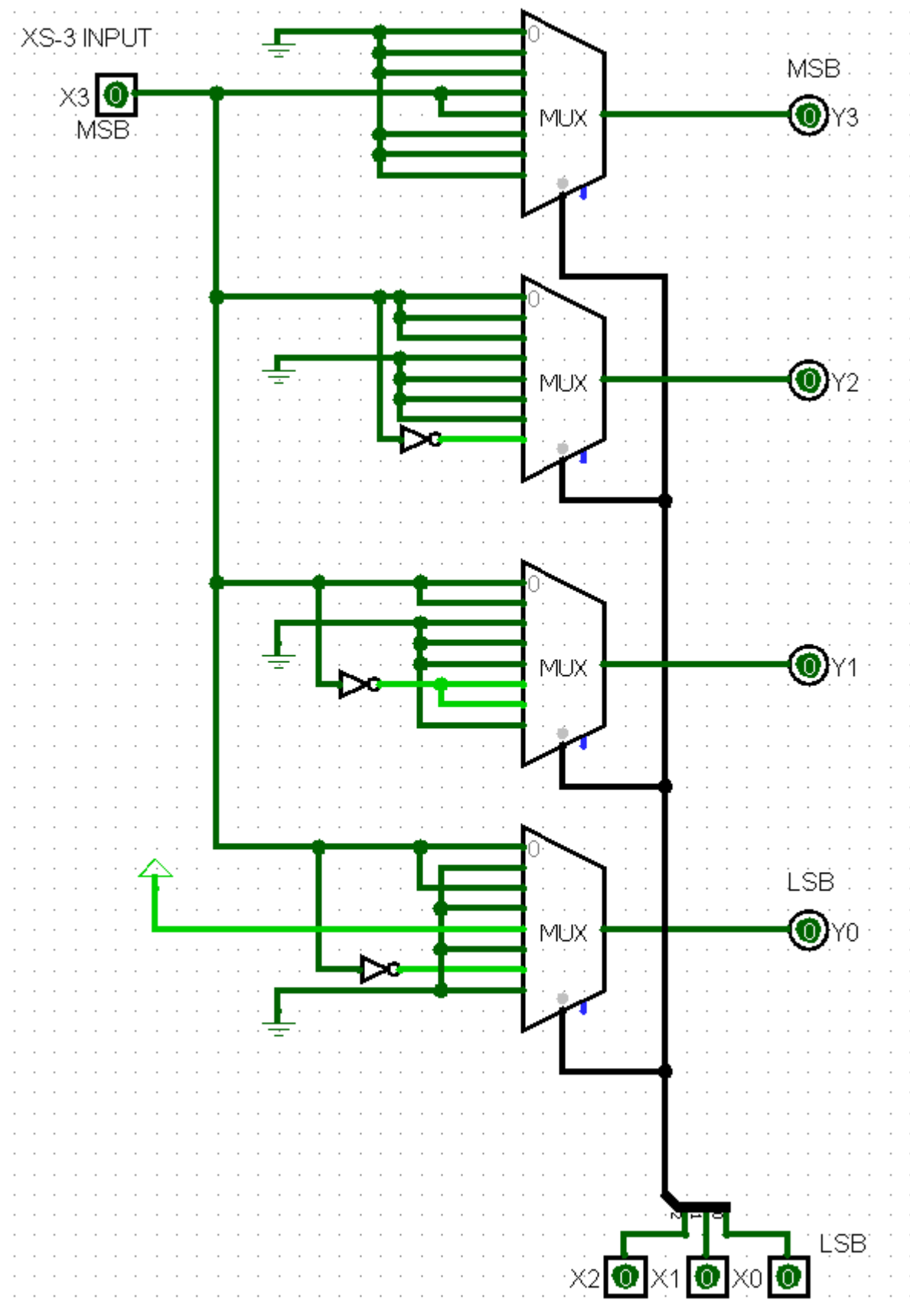

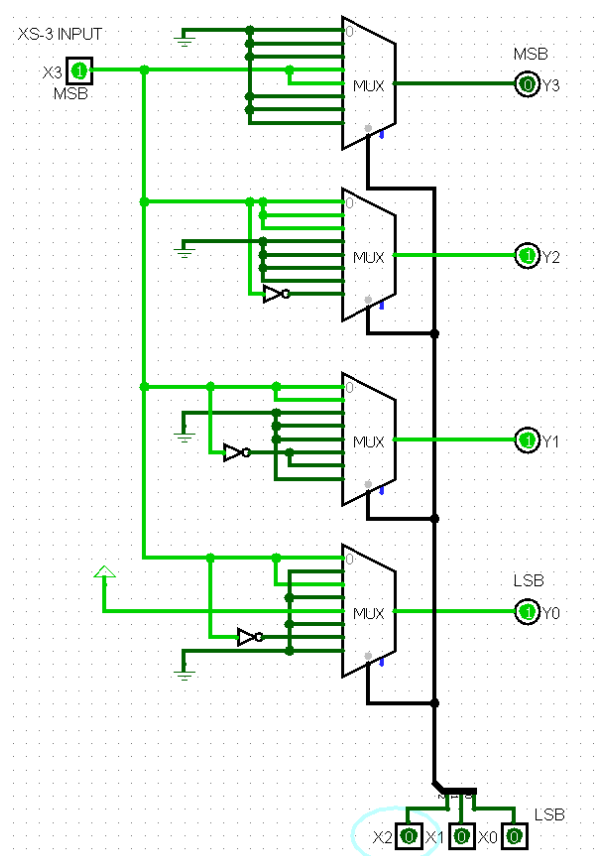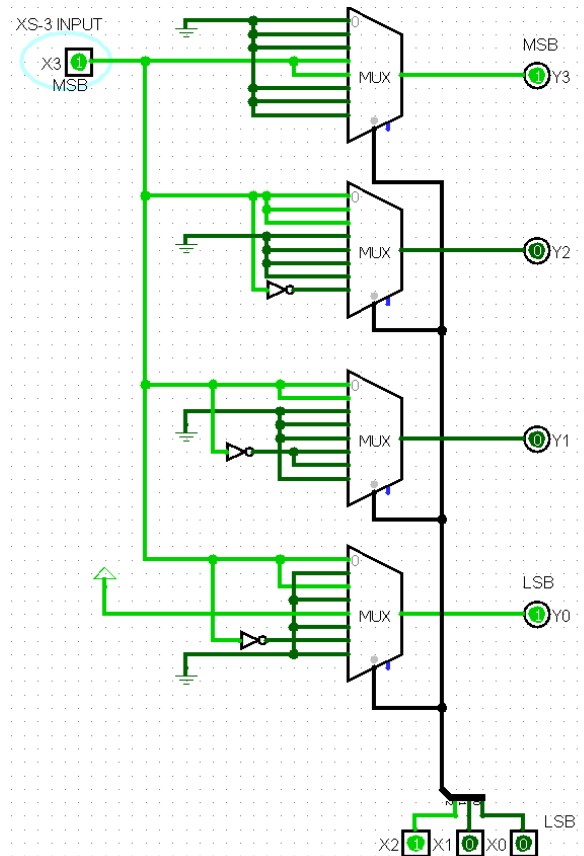RESULT OBTAINED

3. Design a circuit to implement the following functions using (a) 4 to 16 decoder (b) 4 to 1 Multiplexer. Use the Multiplexer and decoder available in Plexers library in logisim.

XOR gates

$$F_1(A,B,C,D) = \sum m (11,12,13,14,15)$$

$$F_2(A,B,C,D) = \sum m (3,7,11,12,13,15)$$

$$F_3(A,B,C,D) = \sum m (3,7,12,13,14,15)$$

Solution:

4 to 16 decoder

TURTH TABLE

A	B	C	D	F1
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

A	B	C	D	F2
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

A	B	C	D	F3
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

KMAP

Output:

Format:

C, D

		00	01	11	10
A, B	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	1	0

$ACD + AB$

Output:

Format:

C, D

		00	01	11	10
A, B	00	0	0	1	0
	01	0	0	1	0
	11	1	1	1	0
	10	0	0	1	0

$CD + AB\bar{C}$

Output:




Format:







C, D

		00	01	11	10
A, B	00	0	0	1	0
	01	0	0	1	0
	11	1	1	1	1
	10	0	0	0	0

$\bar{A}CD + AB$

EXPLAIN

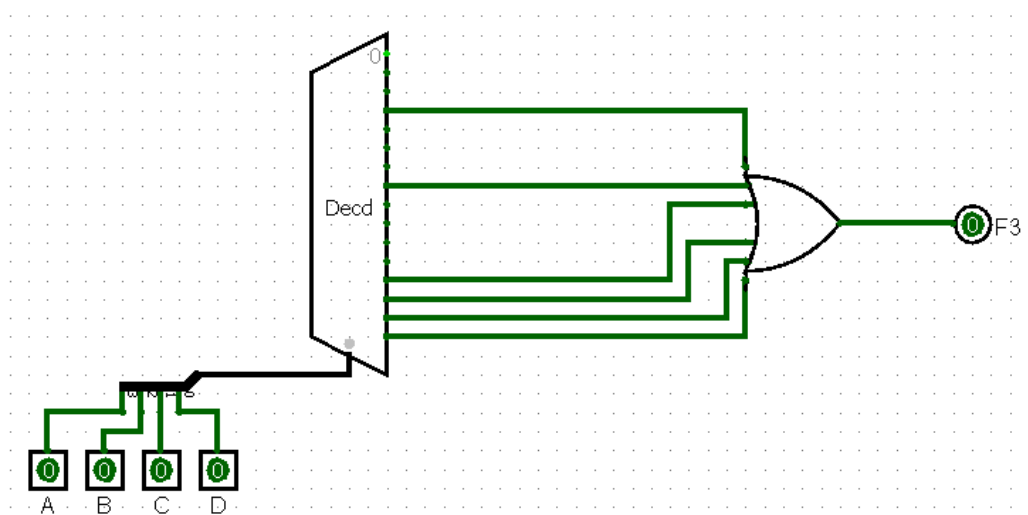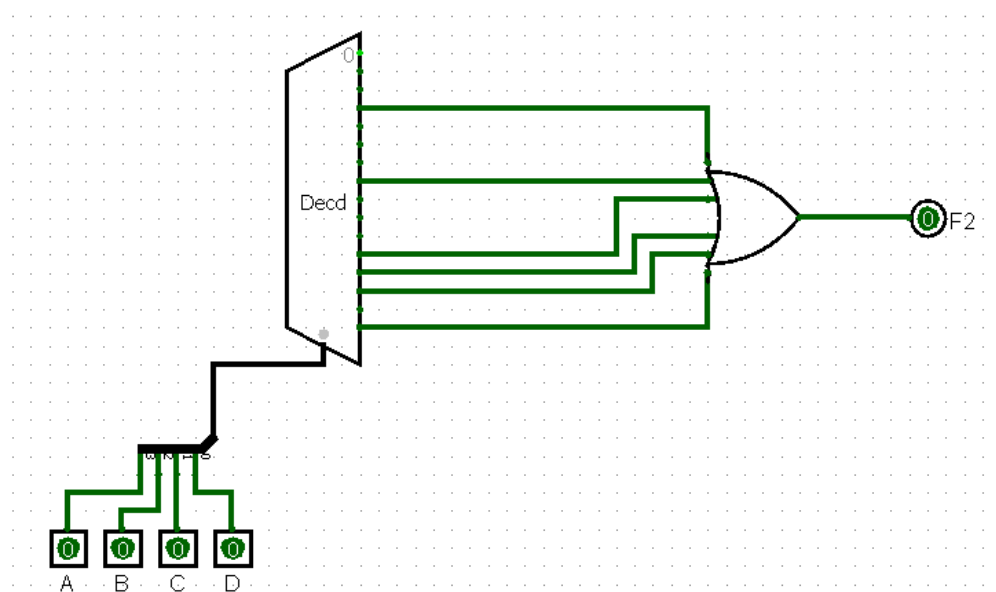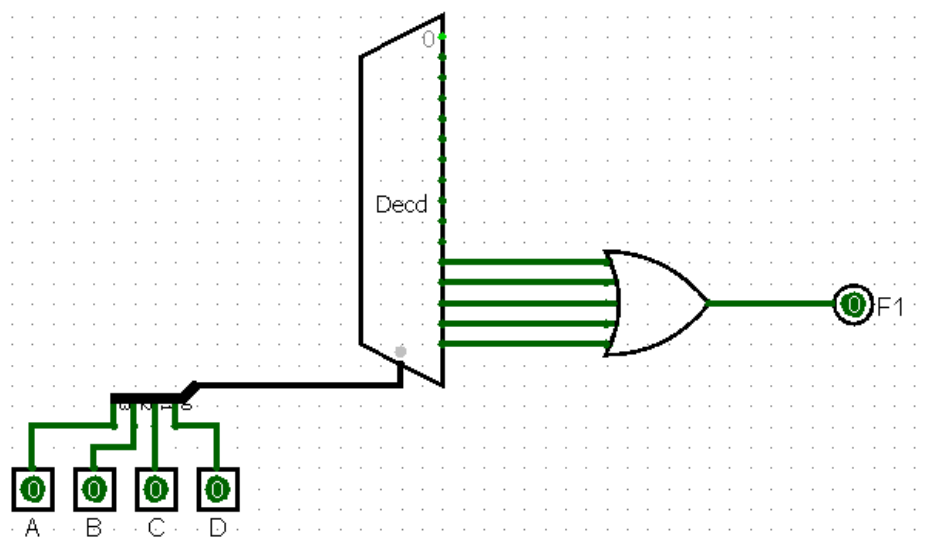CIRCUIT

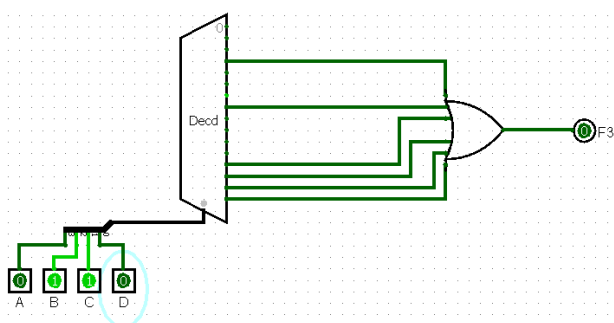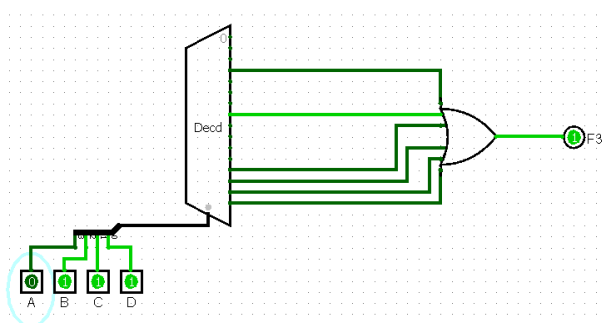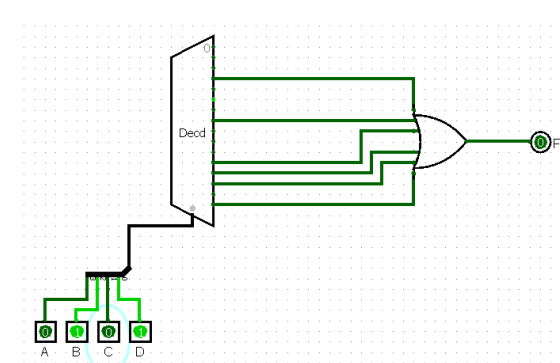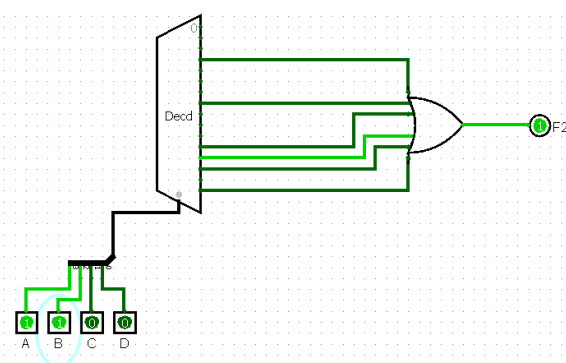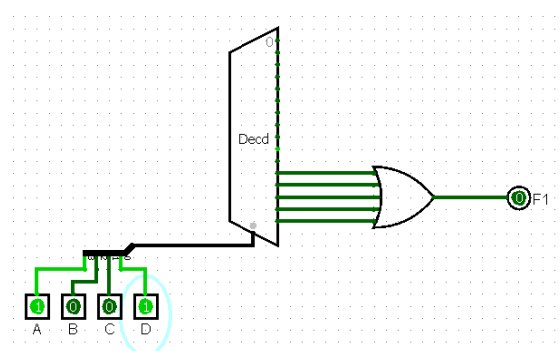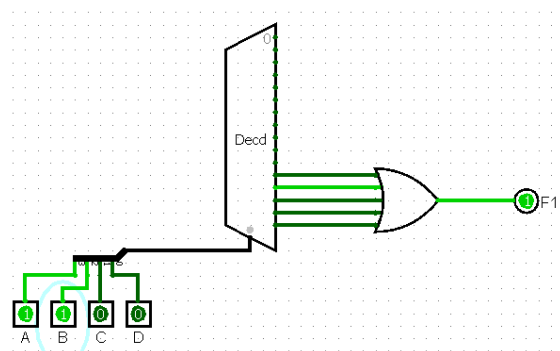RESULT OBTAINED

4 to 1 Multiplexer

TRUTH TABLE

A	B	C	D	F1
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

A	B	C	D	F2
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

A	B	C	D	F3
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

KMAP

Output:

Format:

C, D

		00	01	11	10
A, B	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	1	0

$ACD + AB$

Output:

Format:

C, D

		00	01	11	10
A, B	00	0	0	1	0
	01	0	0	1	0
	11	1	1	1	0
	10	0	0	1	0

$CD + ABC$




Output:

Format:

A, B

		00	01	11	10
C, D	00	0	0	1	0
	01	0	0	1	0
	11	1	1	1	0
	10	0	0	1	0

$AB + CD\bar{A}$

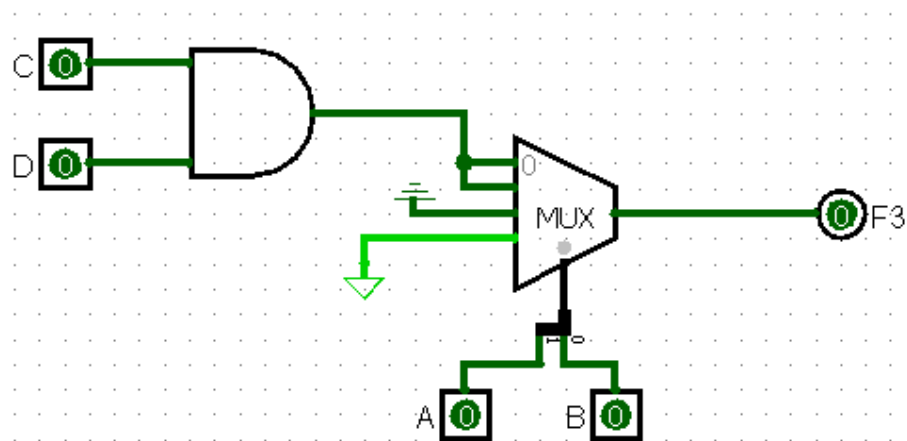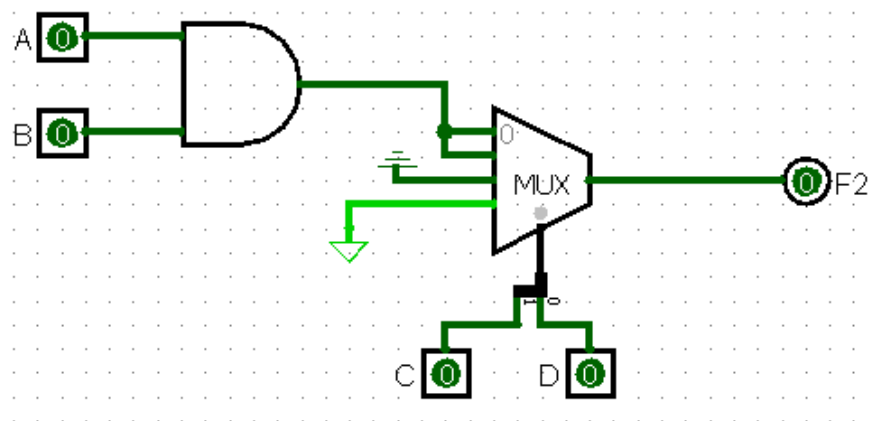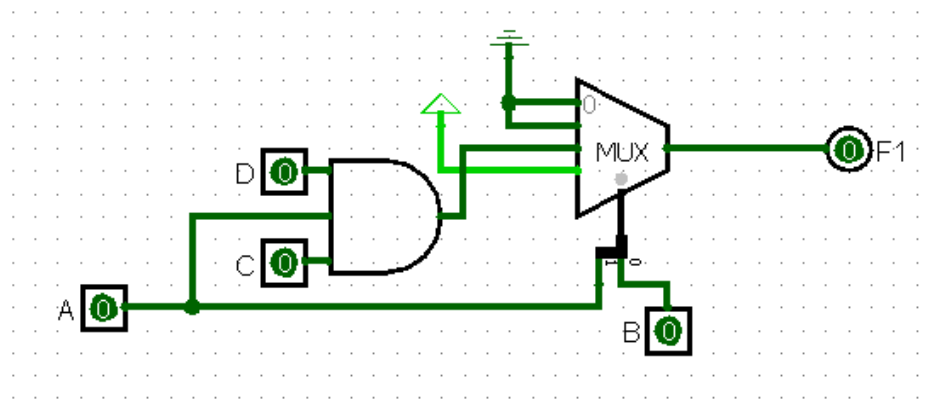CIRCUIT

4. Design a circuit to implement the following function using 16 to 1 Multiplexer. . Use the Multiplexer available in Plexers library in logisim. Solution:

$$F = A'B'C'D'(R'+S) + AB'C'D' + A'B'C'D + ABC'DQR + AB'C'D + A'B'CD (Q'+T) + ABCDS'T + AB'CD + A'BCD$$


Solution:



EXPLAIN

The selector lines can be used as ABCD respectively and the corresponding expression can be found by simply mapping it with the terms given in the question.

For example $\sim A \sim B \sim C \sim D$ is the first input line so we can give $(\sim R + S)$ as the input and that will result in the following term.

CIRCUIT

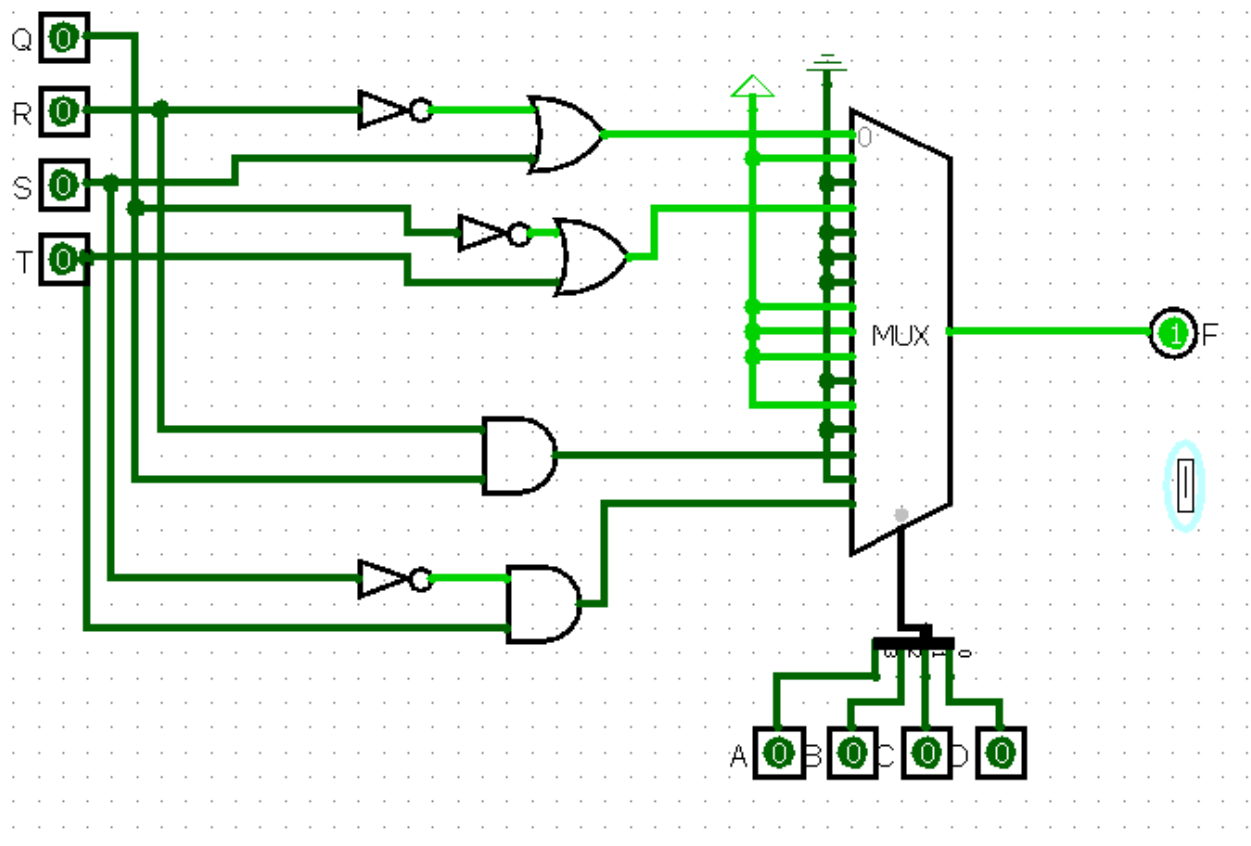

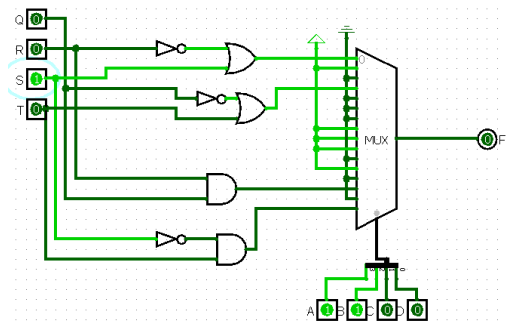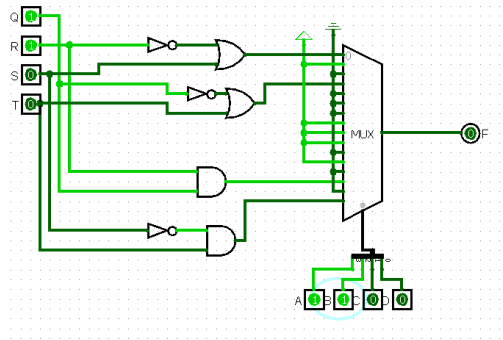RESULT OBTAINED

5. Implement (a) 4 bit controllable adder/subtractor (b) 8 bit controllable adder/subtractor.

Use the Adder available in Arithmetic library in logisim.

Solution:

4 bit controllable adder/subtractor



TURTH TABLE


A3	A2	A1	A0	SUB	B3	B2	B1	B0	COUT	S3	S2	S1	S0
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	0	1	1	0	0	0	1	1
0	0	0	0	0	0	1	0	0	0	0	1	0	0
0	0	0	0	0	0	1	0	1	0	0	1	0	1
0	0	0	0	0	0	1	1	0	0	0	1	1	0
0	0	0	0	0	0	1	1	1	0	0	1	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	0	1	0	1
0	0	0	0	0	1	0	1	0	0	0	1	1	0
0	0	0	0	0	1	0	1	1	0	0	1	1	1
0	0	0	0	0	1	1	0	0	0	0	1	0	0
0	0	0	0	0	1	1	0	1	0	0	1	0	1
0	0	0	0	0	1	1	1	0	0	0	1	1	0
0	0	0	0	0	1	1	1	1	0	0	1	1	1
0	0	0	0	1	0	0	0	0	0	1	0	0	0
0	0	0	0	1	0	0	0	1	0	1	0	0	1
0	0	0	0	1	0	0	1	0	0	1	0	1	0
0	0	0	0	1	0	0	1	1	0	1	0	1	1
0	0	0	0	1	0	1	0	0	0	1	0	1	0
0	0	0	0	1	0	1	1	0	0	1	0	1	1
0	0	0	0	1	0	1	1	1	0	1	0	1	1
0	0	0	0	1	1	0	0	0	0	1	1	0	0
0	0	0	0	1	1	0	0	1	0	1	1	0	1
0	0	0	0	1	1	0	1	0	0	1	1	1	0
0	0	0	0	1	1	0	1	1	0	1	1	1	1
0	0	0	0	1	1	1	0	0	0	1	1	0	0
0	0	0	0	1	1	1	0	1	0	1	1	0	1
0	0	0	0	1	1	1	1	0	0	1	1	1	1

... 256 VALUES

EXPLAIN


Subtraction can be done using 2s complement. Which is nothing but 1s compliment + 1. For subtraction we pass the cin as 1 and we take 1 XOR with the input bits which is to be subtracted. This results in 1's complement to this the adder adds 1 (cin) which results in 2's complement.

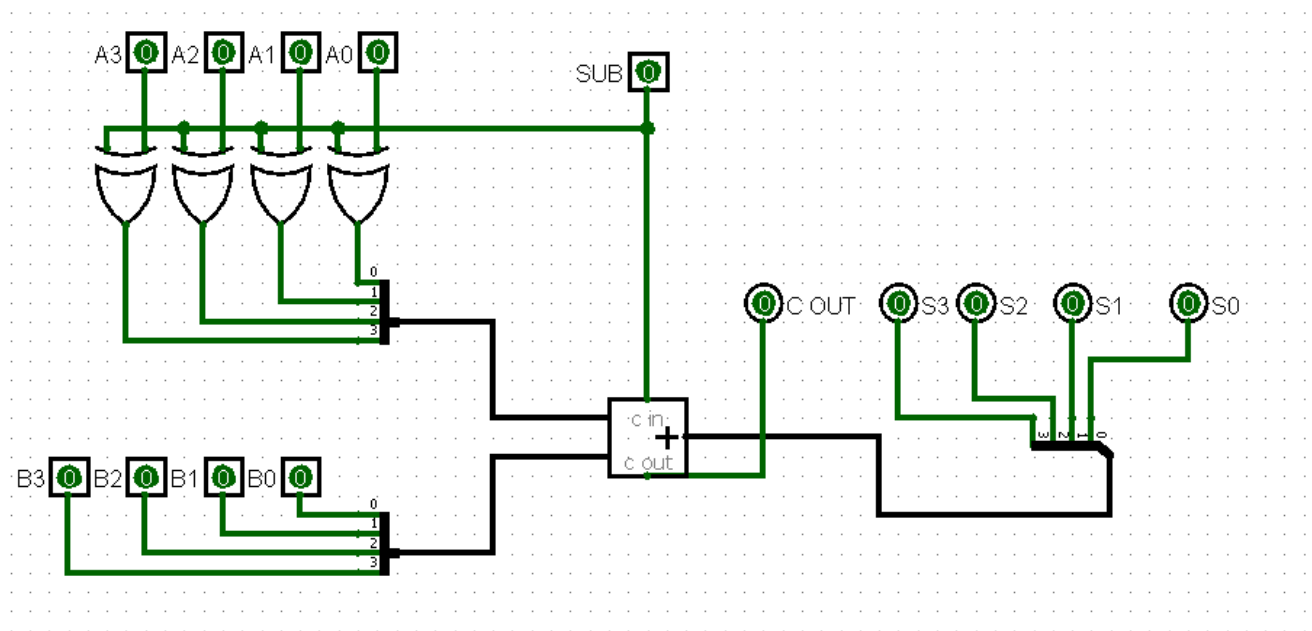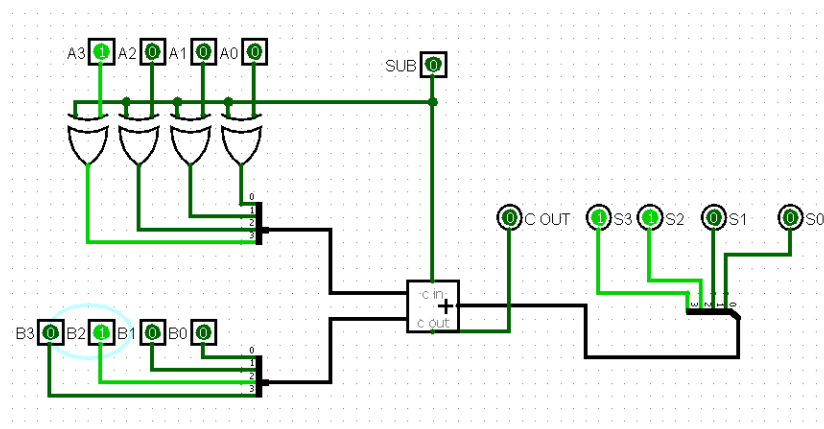CIRCUITRESULT OBTAINED

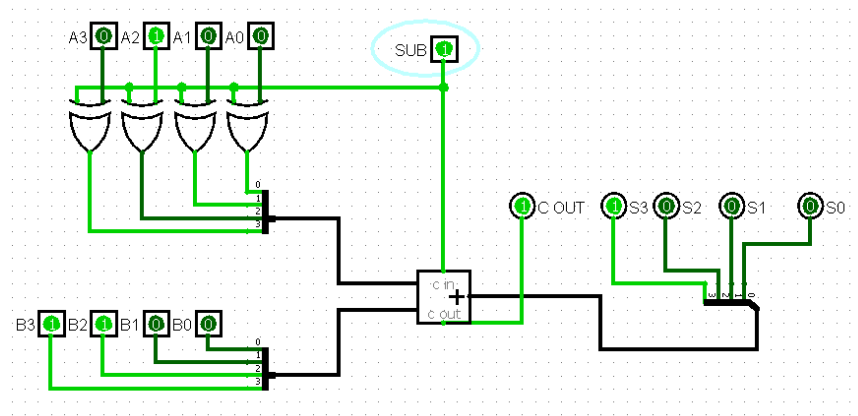

8 bit controllable adder/subtractor

CIRCUIT

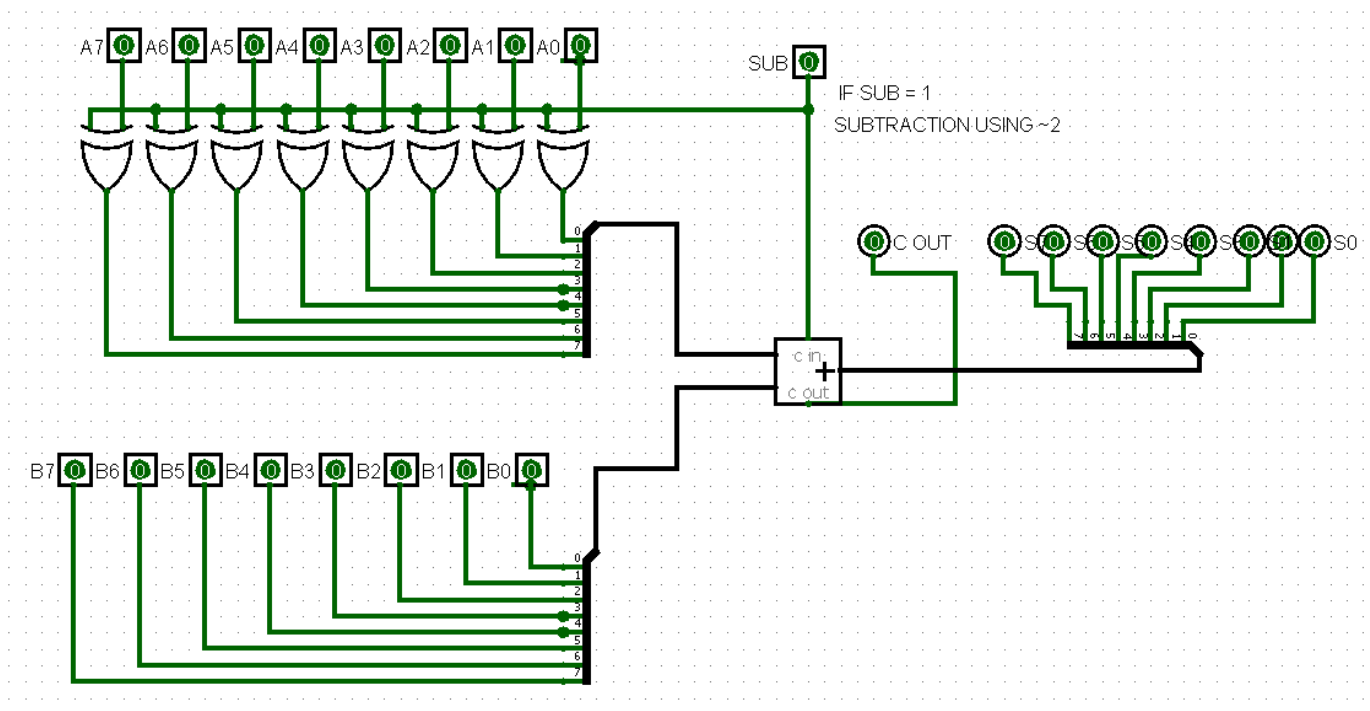

RESULT OBTAINED

